



Lecture 28: Phasors and Impedance

OBJECTIVES:

1. Understand what a Phasor is and how to do phasor math
2. Understand how to apply connection and device constraints with phasors
3. Understand the concept of impedance

READING

Required : Textbook, section 8.1–8.2, pages 379–391

Optional :

1 Introduction

Over the next several lessons, we will start looking at *Steady-state Sinusoidal responses* of circuits. Previously we have been looking at transient responses, so we are shifting gears a little bit. In order to make our analysis easier, we will employ the technique of a phasor analysis. What we will learn today is that a Phasor is just a way of representing a complex number and that they can make some of our math much easier.

2 Phasor Basics

To begin our look at phasors, we start with Euler's identity:

$$e^{j\theta} = \cos \theta + j \sin \theta$$

This is just a complex number of the form $a + jb$ but with a magnitude of 1. We can multiply Euler's equation by a constant to represent any complex number:

$$Ae^{j\theta} = A \cos \theta + j A \sin \theta$$

From here we can recognize:

$$A \cos \theta = \mathbf{Re}[Ae^{j\theta}]$$

$$A \sin \theta = \mathbf{Im}[Ae^{j\theta}]$$

This relationship is shown graphically in Figure 1

We can take advantage of this relationship to simplify some of our calculations.

What happens if we apply the equations above to a more general sinusoid like $A \cos(\omega t + \phi)$?

SOLUTION

ECE231: Electrical Circuits and Systems I - Block III Lecture 28: Phasors and Impedance

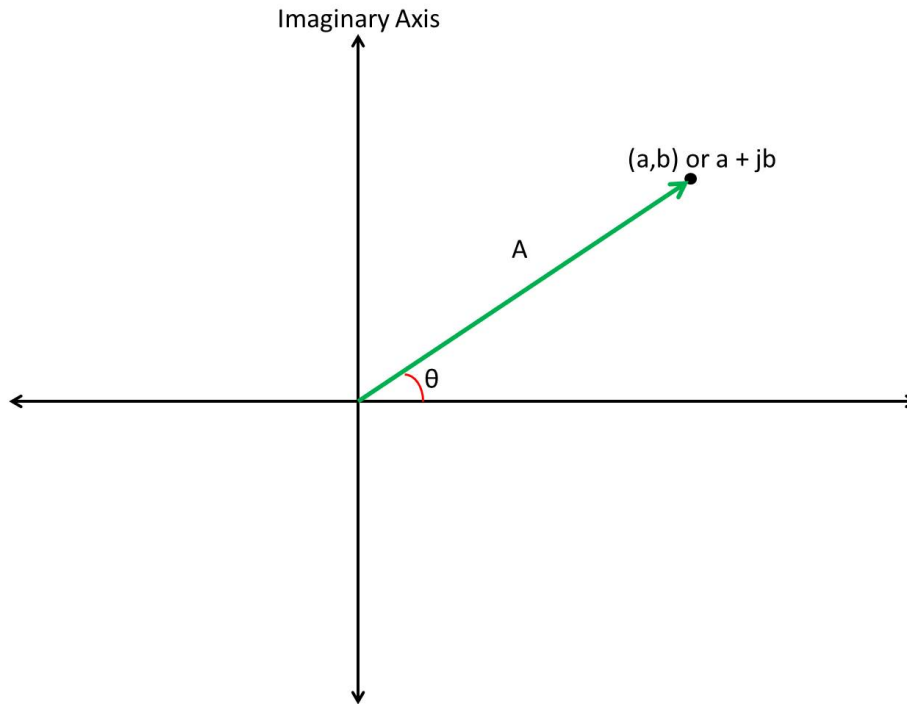


Figure 1: Phasor Diagram

$$A \cos(\omega t + \phi) = A \operatorname{Re} [e^{j(\omega t + \phi)}]$$

$$A \operatorname{Re} [e^{j(\omega t + \phi)}] = A \operatorname{Re} [e^{j\omega t} e^{j\phi}]$$

*If we suppress the **Re** and let $\mathbf{A} = Ae^{j\phi}$ we can rewrite this as*

$$A \operatorname{Re} [e^{j\omega t} e^{j\phi}] = \mathbf{A} e^{j\omega t}$$

We call \mathbf{A} the phasor representation of a sinusoid. Notice that the phasor carries information about the magnitude and phase of the sinusoid, but the frequency information is entirely suppressed. Also note that we could write \mathbf{A} as

$$\mathbf{A} = A \cos \phi + jA \sin \phi$$

We can also use the following notation for \mathbf{A}

$$\mathbf{A} = A \angle \phi$$

SOLUTION

ECE231: Electrical Circuits and Systems I - Block III Lecture 28: Phasors and Impedance

Example 1— Write the phasor representation of the following sinusoids (write in both polar and rectangular form):

- $20 \cos(150t - 60^\circ)$
- $10 \cos(1000t + 180^\circ)$
- $-4 \cos 3t + 3 \cos(3t - 90^\circ)$

Handwritten solution for Example 1:

- $20 \cos(150t - 60^\circ)$
 $20 \angle -60^\circ = 20 \cos\left(-\frac{\pi}{3}\right) + j 20 \sin\left(-\frac{\pi}{3}\right)$
 $= 10 - j 17.3$
- $10 \cos(1000t + 180^\circ)$
 $10 \angle 180^\circ = -10 \angle 0^\circ = -10 + j 0$
- $-4 \cos(3t) + 3 \cos(3t - 90^\circ)$
 $-4 \angle 0^\circ + 3 \angle -90^\circ = -4 + j 0 + 0 - j 3$
 $= -4 - j 3 = \sqrt{4^2 + 3^2} \angle (180^\circ - \tan^{-1}(\frac{3}{4}))$
 $= 5 \angle -143^\circ$

A phasor diagram is shown for the third sinusoid, illustrating the vector addition of -4 and $-j3$ to find the resultant magnitude of 5 and angle of -143° .

Example 2—Convert the following phasors to sinusoids (assume frequency = ω):

- $\mathbf{V} = 169 \angle -45^\circ$
- $\mathbf{V} = 10 \angle 90^\circ + 66 - j10$
- $\mathbf{I} = 15 + j5 + 10 \angle 180^\circ$

Handwritten solution for Example 2:

- $\bar{\mathbf{V}} = 169 \angle -45^\circ$
 $v(t) = 169 \cos(\omega t - 45^\circ)$
- $\bar{\mathbf{V}} = 10 \angle 90^\circ + 66 - j10$
 $v(t) = 66 \cos(\omega t)$
- $\bar{\mathbf{I}} = 15 + j5 + 10 \angle 180^\circ =$
 $i(t) = 7.07 \cos(\omega t + 45^\circ)$

A phasor diagram is shown for the third phasor, illustrating the vector addition of 15 and $j5$ to find the resultant magnitude of 7.07 and angle of 45° .

SOLUTION

ECE231: Electrical Circuits and Systems I - Block III Lecture 28: Phasors and Impedance

3 Important Properties of Phasors

When using the following properties to analyze circuits it is important to always remember all our sinusoids (phasors) have to be the same frequency! We are also only looking at steady state sinusoids!

3.1 Additive Property

If we have two phasors $\mathbf{A} = A\angle\phi_A$ and $\mathbf{B} = B\angle\phi_B$ and we want to add them, we must first convert to rectangular form:

$$A\angle\phi_A = A \cos \phi_A + jA \sin \phi_A$$

$$B\angle\phi_B = B \cos \phi_B + jB \sin \phi_B$$

We can now use rules of complex addition to add these complex numbers

$$\mathbf{A} + \mathbf{B} = [A \cos \phi_A + B \cos \phi_B] + j[A \sin \phi_A + B \sin \phi_B]$$

Finally, we can convert back to polar form,

Example 3 –Textbook Exercise 8-3. Write the two signals below in phasor form, then add them.

$$i_1(t) = 100 \cos(2000t) \text{ mA}$$

$$i_2(t) = 50 \cos(2000t - 60^\circ) \text{ mA}$$

$$\mathbf{I}_1 = 100\angle 0^\circ \text{ mA} = 100 + j0 \text{ mA}$$

$$\mathbf{I}_2 = 50\angle -60^\circ \text{ mA} = 25 - j43.3 \text{ mA}$$

$$\mathbf{I}_1 + \mathbf{I}_2 = [100 + 25] + j[0 - 43.3] = 125 - j43.3 \text{ mA}$$

To convert back to polar form

$$|\mathbf{I}_1 + \mathbf{I}_2| = \sqrt{125^2 + (-43.3)^2} = 132.3 \text{ mA}$$

$$\angle \mathbf{I}_1 + \mathbf{I}_2 = \tan^{-1} \left(\frac{-43.3}{125} \right) = -19.1^\circ$$

*Note: Be careful with the angle calculation... Depending on which quadrant you are in you the calculation can change... In quadrant 1 or 4, you can just take \tan^{-1} ... In quadrant 2, you have to take $180^\circ - \tan^{-1}$ In quadrant 3, you will take $-(180^\circ - \tan^{-1})$. **Show some examples***

$$\mathbf{I}_1 + \mathbf{I}_2 = 132.3\angle -19.1^\circ$$

SOLUTION

ECE231: Electrical Circuits and Systems I - Block III Lecture 28: Phasors and Impedance

3.2 Multiplication and Division

Good News! Multiplication and Division are a piece of cake with Phasors....

Recall that phasors are just complex exponentials and to multiply exponentials we follow the simple rule shown below:

$$Ae^{j\phi_A} \times Be^{j\phi_B} = AB e^{j(\phi_A + \phi_B)}$$

So for phasors we can write:

$$A\angle\phi_A \times B\angle\phi_B = AB\angle(\phi_A + \phi_B)$$

Example 4– Multiply the following two phasors:

$$\mathbf{A} = 10\angle 25^\circ$$

$$\mathbf{B} = 7\angle 15^\circ$$

$$\mathbf{AB} = 7 \times 10\angle(25^\circ + 15^\circ) = 70\angle 40^\circ$$

Division is very similar to multiplication:

$$\frac{A\angle\phi_A}{B\angle\phi_B} = \frac{A}{B}\angle(\phi_A - \phi_B)$$

3.3 Derivative Property

We have already seen that the derivative of a sinusoid is another sinusoid of the same frequency; this allows us to use phasors to describe their relationship. Lets start by recalling that a sinusoid $v(t)$ is related to its phasor $\mathbf{V} = V\angle\phi_V$ by

$$v(t) = \mathbf{Re}\{\mathbf{V}e^{j\omega t}\}$$

What happens when we take the time derivative of this expression?

$$\frac{\partial v(t)}{\partial t} = \frac{\partial}{\partial t} \mathbf{Re}\{\mathbf{V}e^{j\omega t}\}$$

*The differential on the right side of the equation can be moved inside the **Re** and the derivative taken:*

$$\frac{\partial v(t)}{\partial t} = \mathbf{Re}\left\{\frac{\partial \mathbf{V}e^{j\omega t}}{\partial t}\right\}$$

This gives us

$$\frac{\partial v(t)}{\partial t} = \mathbf{Re}\{j\omega \mathbf{V}e^{j\omega t}\}$$

*Since for phasors we suppress the **Re** and the frequency dependence ($e^{j\omega t}$), we can take a derivatives in the phasor domain by just multiplying by $j\omega$.*

Given that we can take a derivative in the phasor domain by multiplying by $j\omega$, we also know that:

$$j\omega \mathbf{V} = \left(\omega e^{j90^\circ}\right) (V e^{j\phi}) = \omega V e^{j(\phi+90^\circ)}$$

So the derivative scales the amplitude by ω and shifts the phase by 90° .

SOLUTION

ECE231: Electrical Circuits and Systems I - Block III Lecture 28: Phasors and Impedance

4 Introduction to Circuit Analysis with Phasors

In this section we will introduce how we can make circuit analysis easier by using phasors. You have to remember that this analysis only applies to circuits that are excited by single frequency sinusoids and are in steady state. This does not replace the transient analysis we have already learned.

4.1 Connection Constraints

As a reminder when we talk about connection constraints we are talking about **KVL** and **KCL**. When we looked at circuits with sinusoidal forcing functions after they had reached steady state (natural response had decayed to zero), we observed that the forced response was also a sinusoid with the same frequency as the forcing function. This means we could write a KVL equation around a loop that might look like:

$$V_1 \cos(\omega t + \phi_1) + V_2 \cos(\omega t + \phi_2) + V_3 \cos(\omega t + \phi_3) + \dots = 0$$

Where each voltage can have different amplitudes and phases, but they must have the same frequency, ω . If we were to write the equation above in phasor form we would get:

$$V_1 \angle \phi_1 + V_2 \angle \phi_2 + V_3 \angle \phi_3 + \dots = 0$$

This tells us that phasor voltages around a loop sum to zero; this is a phasor form of KVL. You can also apply this to KCL; phasor current at a node must sum to zero.

4.2 Device Constraints

By device constraints we are referring to the $i-v$ characteristics of devices (resistors, capacitors and inductors). Lets look at how phasor analysis might help us here. In the analysis below all currents and voltages are sinusoids with the following forms

$$v(t) = \cos(\omega t + \phi)$$

$$i(t) = \cos(\omega t + \phi)$$

Resistors: The device constraint for resistors is just Ohm's law

$$v_R(t) = i_R(t)R$$

If we write this in Phasor form we get

$$V_R \angle \phi_V = I_R \angle \phi_I \times R$$

It should be obvious that $\phi_V = \phi_I$, which means the voltage across a resistor and the current through the same resistor have the same phase angle (or are *in phase*).

Capacitors – The device constraint for a capacitor is:

$$i_c(t) = C \frac{\partial v_c(t)}{\partial t}$$

If we use the derivative property to write this in phasor form we get:

$$I_c \angle \phi_I = j\omega C V_c \angle \phi_V$$

To make this look more like Ohm's law, lets solve for V:

$$V_c \angle \phi_V = \frac{1}{j\omega C} I_c \angle \phi_I$$

Now for some mathemagic.... We know we can multiply anything by 1 without changing the value. We should also recognize that $-j^2 = 1$... If we multiply $\frac{1}{j\omega C}$ by $-j^2$ we get:

$$-j^2 \times \frac{1}{j\omega C} = \frac{-j}{\omega C} = \frac{1}{\omega C} \angle -90^\circ$$

SOLUTION

ECE231: Electrical Circuits and Systems I - Block III Lecture 28: Phasors and Impedance

plugging this back into our equation for \mathbf{V}_c gives us

$$V_c \angle \phi_V = \frac{I_c}{\omega C} \angle (\phi_I - 90^\circ)$$

so

$$\angle \phi_V = \angle (\phi_I - 90^\circ)$$

This tells us that the phase of the voltage across a capacitor lags the current through that capacitor by 90° !

We can simplify the equation above by letting $\mathbf{V}_c = V_c \angle \phi_V$ and $\mathbf{I}_c = I_c \angle \phi_I$. This allows us to write the equation more simply as:

$$\mathbf{V}_c = -\frac{j}{\omega C} \mathbf{I}_c$$

Inductors– The device constraint for an Inductor is:

$$v_L(t) = L \frac{\partial i_L(t)}{\partial t}$$

Like for our capacitor derivation we can use the derivative property to write this in phasor form we get:

$$V_L \angle \phi_V = j\omega L I_L \angle \phi_I$$

Similar to our capacitor development we should know that

$$j\omega L = \omega L \angle 90^\circ$$

Plugging this into the equation above gives:

$$V_L \angle \phi_V = \omega L \angle 90^\circ I_L \angle \phi_I = \omega L I_L \angle (\phi_I + 90^\circ)$$

This tells us that the phase of the voltage across an inductor leads the current through that inductor by 90° !

We can simplify the equation above by letting $\mathbf{V}_L = V_L \angle \phi_V$ and $\mathbf{I}_L = I_L \angle \phi_I$. This allows us to write the equation more simply as:

$$\mathbf{V}_L = j\omega L \mathbf{I}_L$$

A handy way to remember the current and voltage relationships in inductors and capacitors is to use the acronym *ELI the ICE man*.... *E* leads *I* in an inductor... *I* leads *E* in a capacitor.... In older texts books *E* is used for voltage.

SOLUTION

ECE231: Electrical Circuits and Systems I - Block III Lecture 28: Phasors and Impedance

5 Impedance

We spent the last section deriving $i-v$ relationships in the phasor domain, but what has that really done for us? If we look closely we will notice all the $i-v$ relationships in the above sections we will notice they all have the form:

$$\mathbf{V} = \mathbf{I}Z$$

where \mathbf{V} and \mathbf{I} are phasor voltage and current.

So for steady state sinusoidal circuits we can use a modified version of Ohm's law to analyze circuits with resistors, capacitors and inductors... No differential equations to be dealt with....

What is Z ? Z is device impedance and is shown below for each circuit device:

$$Z_R = R$$


$$Z_C = -\frac{j}{\omega C} = \frac{1}{j\omega C}$$

$$Z_L = j\omega L$$

Note: Impedances add just like resistances!

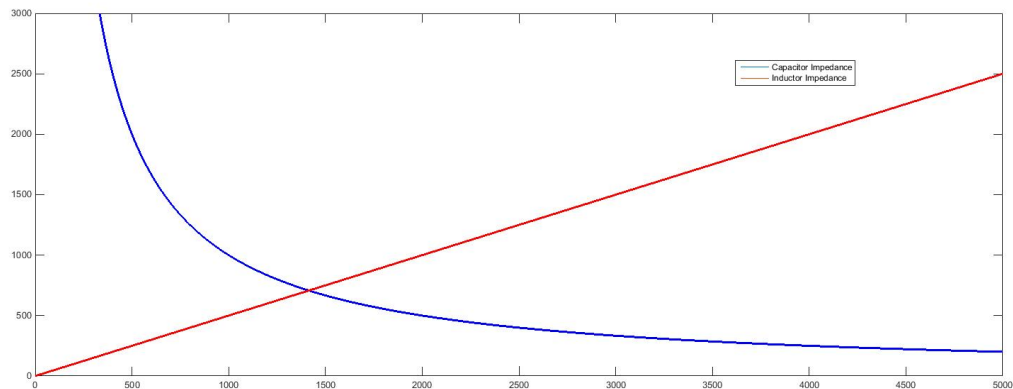5.1 Frequency and Impedance

From the equations above, it should be obvious that the impedance of a resistor is not affected by the frequency of the driving signal, however, the impedance of capacitors or inductors is affected. To understand this effect, let's plot the impedance of a $1 \mu F$ capacitor and a $500 mH$ inductor:



This is consistent with what we know about capacitors and inductors for DC ($\omega = 0$). A capacitor is an open circuit ($Z = \infty$) and an inductor is a short ($Z = 0$).

SOLUTION

ECE231: Electrical Circuits and Systems I - Block III Lecture 28: Phasors and Impedance

Example 5— For the circuit shown in Figure 2, find the impedance of the box if $v(t) = 50 \cos(500t)$ V and $i(t) = 4 \cos(500t - 60^\circ)$ A.

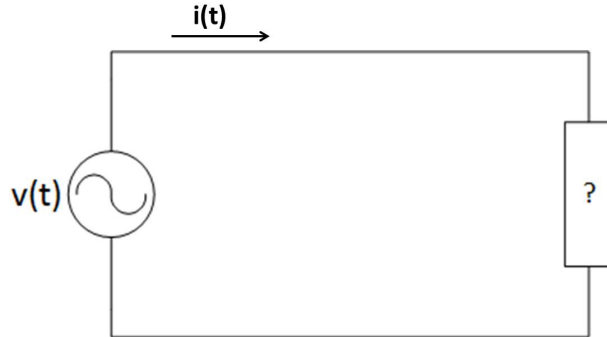


Figure 2: Circuit to accompany Example 5

Step 1 - Write voltage and current as phasors

$$\mathbf{V} = 50\angle 0^\circ = 50$$

$$\mathbf{I} = 4\angle(-60^\circ) = 2 - j3.46$$

Step 2 - Use $\mathbf{V} = \mathbf{I}Z$ to find the impedance

$$Z = \frac{\mathbf{V}}{\mathbf{I}} = \frac{50}{4\angle(60^\circ)} = 12.5\angle 60^\circ = 6.25 + j10.8 \, \Omega$$