



Lecture 34: Filters II – Low and High Pass Filters

OBJECTIVES:

1.

READING

Required : Filters Handout (Available on Sharepoint), pgs 14-34

Optional :

1 Introduction

Last lesson we talked about transfer functions; this lesson we will discuss filters and what their transfer functions look like. In order to do that, I want to start by giving a few definitions:

Cut-off Frequency, ω_c – The frequency where a filter transitions from the passband to the stopband

Ideal Filter – An ideal filter is a filter whose transfer function turns off abruptly at the cut off frequency, ω_c .

Real Filter – The transfer function of a real filter has a smooth roll off like the ones seen in last lesson

Passband – A filter's passband is the band of frequencies where signals are passed in a circuit

Stopband – The stop band of a filter is the band of frequencies where signals are blocked

For an ideal filter, the value of the cut-off frequency is obvious, but how do we define the cut-off frequency for a real filter?

$$K(\omega_c) = \frac{K_{max}}{\sqrt{2}}$$

In words we would say the cut-off frequency is the frequency where the gain equals the maximum gain divided by the square root of 2.

2 Types of Filters

In this lesson we are going to focus on some simple building block filters. Specifically we will focus on first-order filters; the order of the filter refers to the order of $j\omega$ in the transfer function. Over the next two lessons, we will look at the following four filters:

1. Low Pass Filter (LPF)

SOLUTION

ECE231: Electrical Circuits and Systems I - Block III Lecture 34: Filters II – Low and High Pass Filters

2. High Pass Filter (HPF)
3. Band Pass Filter (BPF)
4. Band Reject Filter (BRF)

For each filter type we will examine the transfer function and will discuss how to physically construct the filter. In general, the cut off for a first order filter is not very sharp; you can sharpen the cut-off by cascading filters and thereby creating a higher order filter.

2.1 Low Pass Filters

As the name implies, Low Pass Filters (LPF) pass the low frequencies and block high frequency. Another way to say this is that the *passband* includes frequencies from zero to the cut-off frequency:

$$0 < \omega_{pass} < \omega_c$$

The *stopband* includes any frequency above the cutoff frequency.

The transfer function of a first order LPF is (memorize this form!):

$$H_{LPF}(j\omega) = K \frac{\omega_c}{j\omega + \omega_c}$$

Where K is the gain and ω_c is the cut-off frequency

SOLUTION

ECE231: Electrical Circuits and Systems I - Block III Lecture 34: Filters II – Low and High Pass Filters

Example 1 – Plot the transfer function of


$$H(j\omega) = \frac{20,000}{j\omega + 1000}$$

What is the *passband* gain? What is the cut-off frequency?

First, we need to write the filter transfer function in standard form

$$H(j\omega) = 20 \frac{1000}{j\omega + 1000}$$

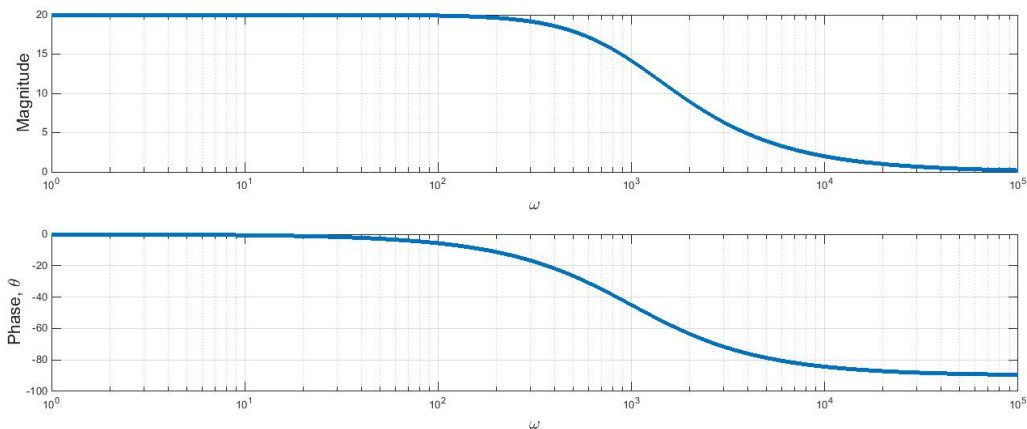From here we can easily see that $K = 20$ and $\omega_c = 1000$



Notice the gain has dropped to 14.14 (0.707×20) at $\omega = 1000$

How would we build this filter? To build a first order LPF, we will start with one of the two circuits in Figure 1. **Note:** Each of these circuits has a gain of 1; a gain greater than 1 requires an amplification stage (think back to op amps).

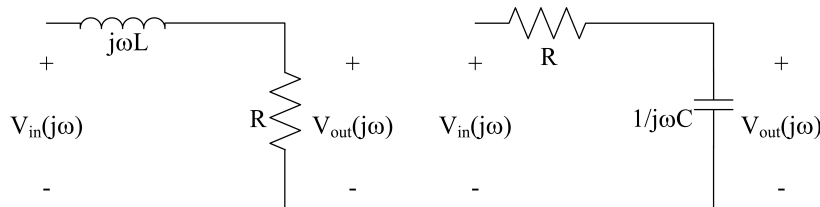


Figure 1: LPF circuits

We can write transfer functions for these circuits:

$$H(j\omega) = \frac{\frac{R}{L}}{j\omega + \frac{R}{L}}$$

$$H(j\omega) = \frac{\frac{1}{RC}}{j\omega + \frac{1}{RC}}$$

We could implement our example above by using a non-inverting op amp with $K = 20$ and letting:

$$\frac{R}{L} = 1000$$

or

$$\frac{1}{RC} = 1000$$

SOLUTION

ECE231: Electrical Circuits and Systems I - Block III Lecture 34: Filters II – Low and High Pass Filters

2.2 High Pass Filters

As the name implies, High Pass Filters (HPF) pass the high frequencies and block low frequency. Another way to say this is that the *passband* includes frequencies from the cut-off frequency to infinity:

$$\omega_c < \omega_{pass}$$

The *stopband* includes any frequency below the cutoff frequency.

The transfer function of a first order HPF is (memorize this form!):

$$H_{HPF}(j\omega) = K \frac{j\omega}{j\omega + \omega_c}$$

Where K is the gain and ω_c is the cut-off frequency

Example 2 – Plot the transfer function of


$$H(j\omega) = \frac{j20\omega}{j\omega + 1000}$$

What is the *passband* gain? What is the cut-off frequency?

First, we need to write the filter transfer function in standard form

$$H(j\omega) = 20 \frac{j\omega}{j\omega + 1000}$$

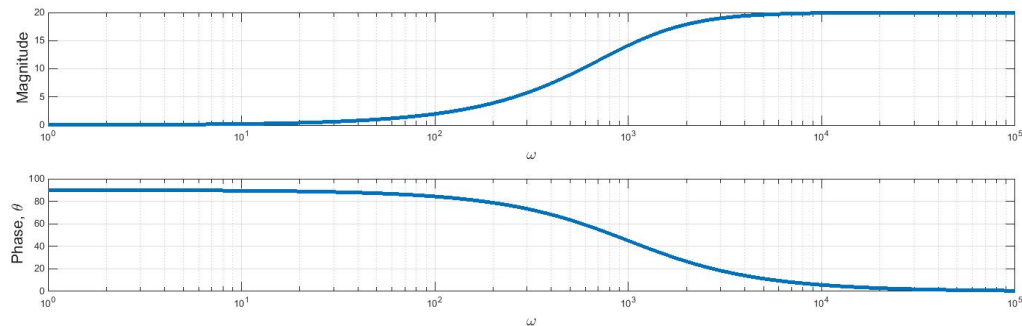From here we can easily see that $K = 20$ and $\omega_c = 1000$



Notice the gain has risen to 14.14 (0.707×20) at $\omega = 1000$

SOLUTION

ECE231: Electrical Circuits and Systems I - Block III Lecture 34: Filters II – Low and High Pass Filters

How would we build this filter? To build a first order HPF, we will start with one of the two circuits in Figure 2. **Note:** Each of these circuits has a gain of 1; a gain greater than 1 requires an amplification stage (think back to op amps).

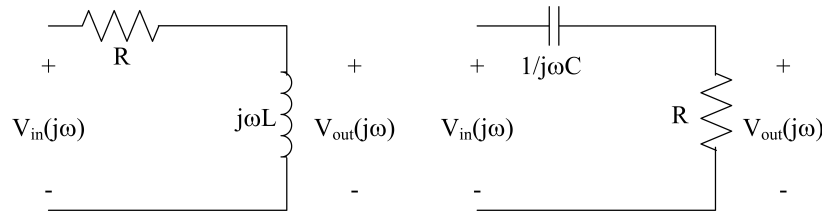


Figure 2: HPF circuits

We can write transfer functions for these circuits:

$$H(j\omega) = \frac{j\omega}{j\omega + \frac{R}{L}}$$

$$H(j\omega) = \frac{j\omega}{j\omega + \frac{1}{RC}}$$

We could implement our example above by using a non-inverting op amp with $K = 20$ and letting:

$$\frac{R}{L} = 1000$$

or

$$\frac{1}{RC} = 1000$$

3 Cascaded Gain Stages with LPF and HPF

We will not use class time to discuss this piece since it is relatively straight forward, but please read section 3.3 of the handout. Take careful notice of the discussions on stage loading!

SOLUTION

ECE231: Electrical Circuits and Systems I - Block III Lecture 34: Filters II – Low and High Pass Filters

4 Active Filters

We can combine the gain stage and the filter stage by using active filters! To do this, we will build our filter around an op amp. We will show how to build filters using an inverting op amp and an RC filter. You can build filters with RL filters and other op amp circuits as well.

Example 3 – Two active filters are shown in Figures 3 and 4; determine the transfer function of each filter and what type filter it is; also specify the gain.

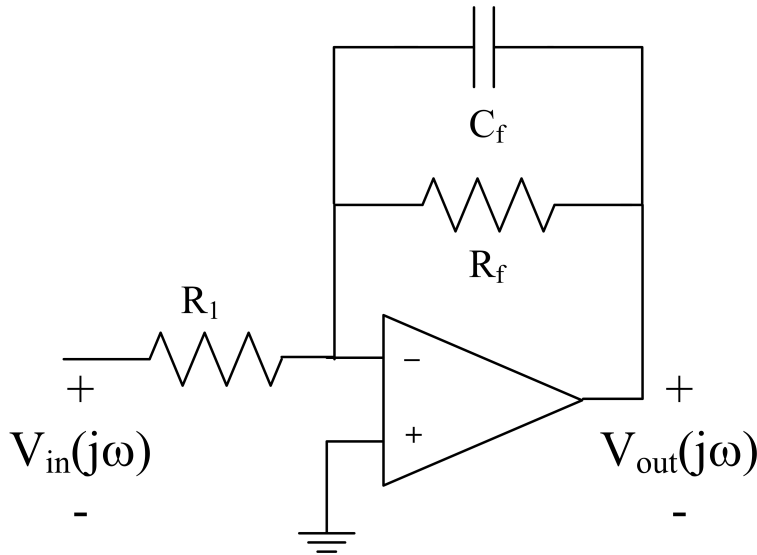


Figure 3: An active filter

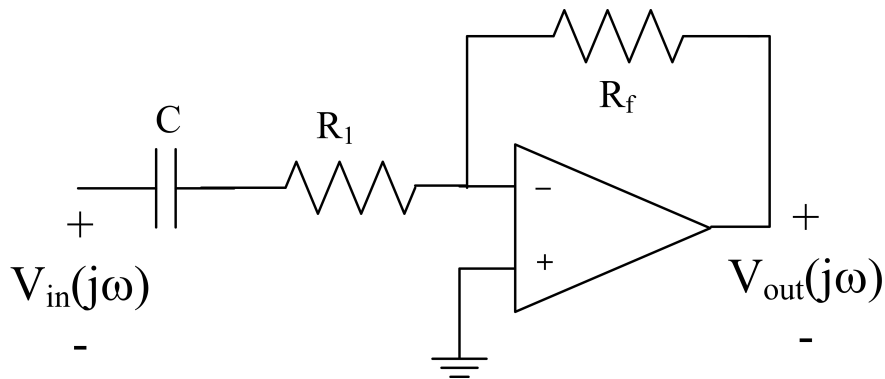


Figure 4: An active filter

SOLUTION

ECE231: Electrical Circuits and Systems I - Block III Lecture 34: Filters II – Low and High Pass Filters

FILTER 1

- WRITE KCL @ AT THE INVERTING NODE

$$\frac{V_{in}(j\omega)}{R_i} + V_{out}(j\omega) \left[\frac{1}{R_f} + j\omega C_f \right] = 0$$

$$V_{out} = \frac{-V_{in}}{R_i \left(\frac{1}{R_f} + j\omega C_f \right)}$$

$$H(j\omega) = \frac{V_{out}}{V_{in}} = \frac{-1}{R_i \left(\frac{1}{R_f} + j\omega C_f \right)} = \frac{-R_f}{R_i} \left[\frac{\frac{1}{R_f C_f}}{j\omega + \frac{1}{R_f C_f}} \right]$$

- THIS IS A LPF

$$K = \frac{-R_f}{R_i}$$

$$\omega_c = \frac{1}{R_f C_f}$$

FILTER 2

$$\frac{V_{in}}{R_i + \frac{1}{j\omega C}} + \frac{V_{out}}{R_f} = 0$$

$$V_{out} = -R_f \left[\frac{V_{in}}{R_i + \frac{1}{j\omega C}} \right]$$

$$H(j\omega) = \frac{V_{out}}{V_{in}} = \frac{-R_f j\omega C}{j\omega C R_i + 1} = \frac{-R_f}{R_i} \left[\frac{j\omega}{j\omega + \frac{1}{C R_i}} \right]$$

- THIS IS A HPF

$$K = \frac{-R_f}{R_i}$$

$$\omega_c = \frac{1}{R_i C}$$

SOLUTION

ECE231: Electrical Circuits and Systems I - Block III Lecture 34: Filters II – Low and High Pass Filters

5 A Quick Primer on Decibels

What is a decibel? In short it is 10 times the logarithm of a power ratio:

$$dB = 10 \log \frac{P_{out}}{P_{in}}$$

The only modification we need to make for our use is that we talk about *voltage gains*. Recall that power is related to voltage squared. This leads us to

$$dB = 10 \log \left[\frac{V_{out}}{V_{in}} \right]^2 = 20 \log \frac{V_{out}}{V_{in}}$$

Most of our magnitude plots will be shown in dB. Figure 5 shows a magnitude plot of $\frac{200}{j\omega + 50}$ in both absolute gain and in dB.

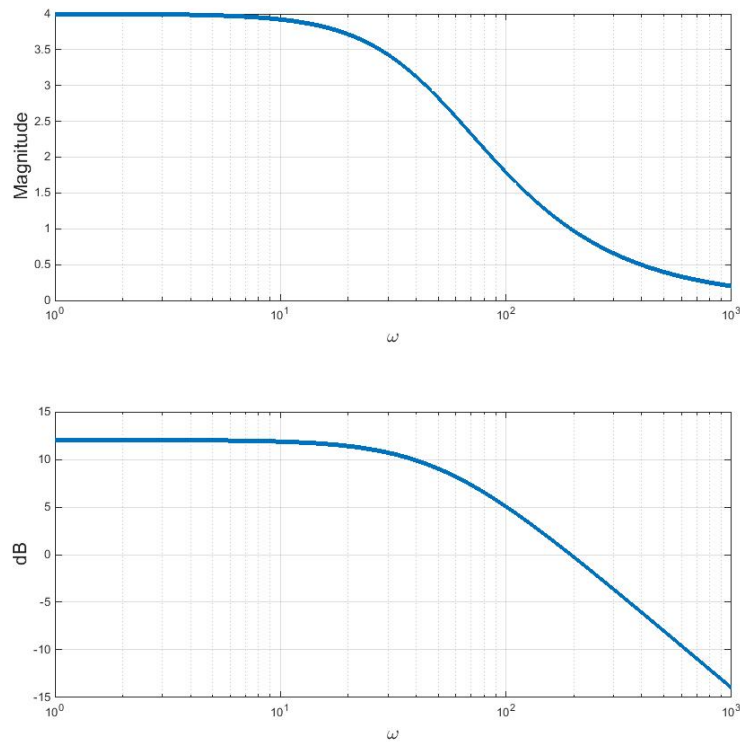


Figure 5: Magnitude response in Gain and dB

Note: At the cut-off frequency, the gain is always 3 dB below the maximum gain (or -3 dB)