



Lecture 20: Capacitors and Inductors

OBJECTIVES:

1. Understand $i-v$ characteristics for capacitors and inductors
2. Understand the capacitors and inductors can store energy
3. Be able to calculate equivalent capacitance and inductance

READING

Required :

- Textbook, section 6.1, 6.2, 6.4, pages 281–293; 301–305

Optional : None

1 Capacitors

A capacitor is a dynamic circuit element that can *store* or *dissipate* charge. To start our discussion of capacitors, we will look at the cartoon of a parallel plate capacitor shown in Figure 1

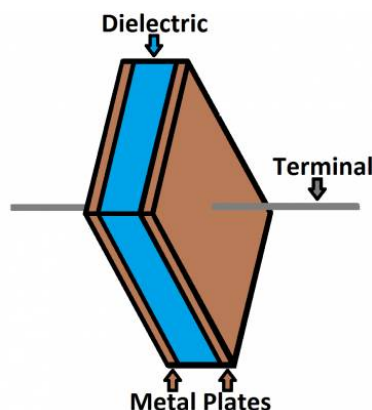


Figure 1: Parallel Plate Capacitor (borrowed from: learn.sparkfun.com)

A parallel plate capacitor is just two metal plates (area, A) separated by a distance, d . If you accumulate a charge, q , on one plate, a negative charge, $-q$ accumulates on the other plate and an electric field exists between the two plates:

SOLUTION

ECE231: Electrical Circuits and Systems I - Spring 2016

Lecture 20: Capacitors and Inductors

$$\vec{\mathcal{E}}(t) = \frac{q(t)}{\epsilon A} \quad (1)$$

where $\vec{\mathcal{E}}(t)$ is the time varying E-field and ϵ is the permittivity of the dielectric. This equation assume d is small compared to A , but this is almost always a good assumption. The units for the E-field are $\frac{V}{m}$ which implies the the E-field is related to a voltage, $v_c(t)$, between the plates:

$$\vec{\mathcal{E}}(t) = \frac{v_c(t)}{d} \quad (2)$$

setting the last two equations equal to each other and solving for charge, $q(t)$ gives:

$$q(t) = \left[\frac{\epsilon A}{d} \right] v_c(t) \quad (3)$$

We will give that bracketed term a special name. We will call it capacitance, C

$$C = \frac{\epsilon A}{d} \quad (4)$$

which allows us to rewrite our charge equation

$$q(t) = C v_c(t) \quad (5)$$

1.1 i - v Characteristic

If we take the time derivative of our last equation we get:

$$\frac{\partial q(t)}{\partial t} = C \frac{\partial v_c(t)}{\partial t} \quad (6)$$

but since $i_c(t) = \frac{\partial q(t)}{\partial t}$ we can rewrite this as

$$i_c(t) = C \frac{\partial v_c(t)}{\partial t} \quad (7)$$

which gives us an i - v relationship for a capacitor. I will leave this derivation to you, but you can write an integral form of this equation as:

$$v_c(t) = v_c(0) + \frac{1}{C} \int_0^t i_c(x) dx \quad (8)$$

where x is just a dummy variable for the integration.

So what does this all mean?

1. A time varying voltage will create current through a capacitor
2. For DC voltage the current is zero (Open Circuit)
3. Capacitor voltage is a continuous function of time

SOLUTION

ECE231: Electrical Circuits and Systems I - Spring 2016

Lecture 20: Capacitors and Inductors

Example 1 –Textbook Exercise 6-1 A $1 \mu F$ capacitor has no voltage across it at $t = 0$. A current flowing through the capacitor is give as:

$$i_c(t) = 2u(t) - 3u(t - 2) + u(t - 4) \mu A \quad (9)$$

Find $v_c(t)$ at $t = 4 s$

Plot $i_c(t)$
 $i_c(t), \mu A$

2
-1

2 4

t, s

WE KNOW

$$v_c(t) = v_c(0) + \frac{1}{C} \int_0^t i_c(x) dx$$
$$v_c(0) = 0$$

Therefore

$$v_c(t) = \frac{1}{1 \times 10^{-6}} \left[\int_0^2 2 dx + \int_2^4 -1 dx \right] \times 10^{-6}$$

REMEMBER μA

$$v_c(t) = \frac{1}{1 \times 10^{-6}} [4 - 2] \times 10^{-6}$$
$$v_c(t) = 2 V$$

SOLUTION

ECE231: Electrical Circuits and Systems I - Spring 2016

Lecture 20: Capacitors and Inductors

1.2 Power and Energy

Power for a capacitor is found using the power law

$$p_c(t) = v_c(t)i_c(t) \quad (10)$$

but using what we learned above, we can write this as

$$p_c(t) = Cv_c(t) \frac{\partial v_c(t)}{\partial t} \quad (11)$$

which can also be written as (using the product rule):

$$p_c(t) = \frac{\partial}{\partial t} \left[\frac{1}{2} C v_c^2(t) \right] \quad (12)$$

Notice that the voltage across the capacitor and the time rate of change of the voltage can have like or opposite signs. For example: $v_c = 5 \text{ V}$ and is decreasing would give opposite signs, while $v_c = 5 \text{ V}$ and is increasing would be like signs.

Why is this important? –

Recall the power law.... A negative result in a power calculation tells us that the device is providing power while a positive result tells us a device is consuming power. Capacitor power can be positive or negative... This means CAPACITORS CAN BOTH BE SOURCES AND SINKS FOR POWER..... A capacitor can store energy!

SOLUTION

ECE231: Electrical Circuits and Systems I - Spring 2016

Lecture 20: Capacitors and Inductors

Example 2 – Textbook Exercise 6-2(a) and 6-4 (a) — The voltage across a $10\ \mu F$ capacitor is

$$v_c(t) = 25 \sin(2000t)u(t)\ V \quad (13)$$

Derive an expression for the current, $i_c(t)$ through the capacitor.

Also find the power for the capacitor.

Is the capacitor absorbing or delivering power at $t = 1\ s$?

Current Expression:

$$i_c(t) = C \frac{\partial v_c(t)}{\partial t} \quad (14)$$

$$i_c(t) = 25 \times 10\ \mu F \frac{\partial}{\partial t} [\sin(2000t)u(t)] \quad (15)$$

$$i_c(t) = 500 \cos(2000t)u(t)\ mA \quad (16)$$

Power:

$$p_c(t) = v_c(t)i_c(t) \quad (17)$$

$$p_c(t) = [25 \sin(2000t)u(t)\ V] \times [500 \cos(2000t)u(t)\ mA] \quad (18)$$

$$p_c(t) = 12.5 \sin(2000t) \cos(2000t)u(t)\ W \quad (19)$$

$$p_c(t) = 6.25 \sin(4000t)u(t)\ W \quad (20)$$

This step relied on this trig identity $\sin(2\theta) = 2 \sin(\theta) \cos(\theta)$ At $t = 1\ s$:

$$p_c(1) = 6.25 \sin(4000)\ W = -4.27\ W \quad (21)$$

Therefore the capacitor is delivering power!

SOLUTION

ECE231: Electrical Circuits and Systems I - Spring 2016

Lecture 20: Capacitors and Inductors

2 Inductors

Our next *dynamic* circuit element to discuss is the inductor. The inductor relies on the fact that when current flows in a wire, a magnetic field is induced around that wire (it follows the right hand rule!). If we were to coil the wire, the magnetic flux would concentrate along the axis of the coil; see Figure 2. The magnetic flux will be proportional to the current and the number of turns of wire:

$$\phi(t) = \frac{\mu N A}{l} i_L(t) \quad (22)$$

where μ is the permeability of the core, l is the length of the coil, and A is the cross sectional area.

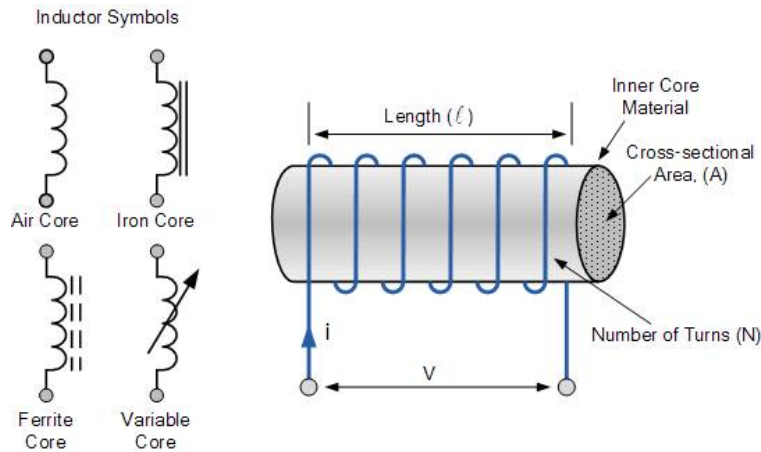


Figure 2: A basic inductor (borrowed from: <http://www.electronics-tutorials.ws>)

We will say that the magnetic flux along the axis of this coil of wire links the turns of the coil and we will define the flux linkage, λ , by

$$\lambda(t) = N\phi(t) \quad (23)$$

We can combine the last 2 equations to get

$$\lambda(t) = \frac{\mu N^2 A}{l} i_L(t) \quad (24)$$

We will now give the proportionality constant above a special name, inductance, and give it the symbol, L :

$$L = \frac{\mu N^2 A}{l} \quad (25)$$

which gives

$$\lambda(t) = L i_L(t) \quad (26)$$

SOLUTION

ECE231: Electrical Circuits and Systems I - Spring 2016

Lecture 20: Capacitors and Inductors

2.1 Inductor i - v Characteristic

On the first day of class we offered the following definition of voltage:

$$v(t) = \frac{\partial \lambda}{\partial t} \quad (27)$$

Combining this with the last equation gives us:

$$v_L(t) = L \frac{\partial}{\partial t} i_L(t) \quad (28)$$

which is the i - v relationship for an inductor. We can also write this integral form:

$$i_L(t) = i_L(0) + \frac{1}{L} \int_0^t v_L(x) dx \quad (29)$$

So what does this all mean?

- 1. A time varying current will create voltage across an inductor*
- 2. For DC current the voltage is zero (Short Circuit)*
- 3. Inductor current is a continuous function of time*

SOLUTION

ECE231: Electrical Circuits and Systems I - Spring 2016 Lecture 20: Capacitors and Inductors

2.2 Power and Energy

Inductor power can be written as:

$$p_L(t) = v_L(t)i_L(t) \quad (30)$$

which using our i - v characteristic, we can rewrite as

$$p_L(t) = Li_L(t)\frac{\partial}{\partial t}i_L(t) = \frac{1}{2}L\frac{\partial}{\partial t}i_L^2(t) \quad (31)$$

The current through the inductor $i_L(t)$ and its time derivative can have like or opposite signs; this means (like a capacitor) that an inductor can be a power source or power sink. When an inductor is *sinking* power, it is storing energy that will be delivered back to the circuit at a later time.

Example 3 – Textbook Exercise 6-6— For $t > 0$, the voltage across the a 4 mH inductor is $v_L(t) = 20e^{-2000t}$ & $i_L(0) = 0$.

Find:

- (a) The current through the inductor for $t > 0$
- (b) The power for $t > 0$?

Current:

$$\begin{aligned} i_L(t) &= i_L(0) + \frac{1}{L} \int_0^t v_L(x) dx \\ i_L(t) &= \frac{1}{4 \times 10^{-3}} \int_0^t 20e^{-2000x} dx \\ i_L(t) &= -\frac{1}{2000 \times 4 \times 10^{-3}} [20e^{-2000x}]_0^t \\ i_L(t) &= 2.5 [1 - e^{-2000t}] \text{ A} \end{aligned}$$

Power:

$$\begin{aligned} p_L(t) &= Li_L(t)\frac{\partial}{\partial t}i_L(t) \\ p_L(t) &= 4 \times 10^{-3} \times 2.5 [1 - e^{-2000t}] \frac{\partial}{\partial t} 2.5 [1 - e^{-2000t}] \\ p_L(t) &= 25 \times 10^{-3} [1 - e^{-2000t}] [2000e^{-2000t}] \\ p_L(t) &= 50 [e^{-2000t} - e^{-4000t}] \text{ W} \end{aligned}$$

SOLUTION

ECE231: Electrical Circuits and Systems I - Spring 2016

Lecture 20: Capacitors and Inductors

Example 4– Textbook Exercise 6-7— For $t < 0$ current through a 100 mH inductor is zero. For $t \geq 0$, the current is $i_L(t) = 20e^{-2000t} - 20e^{-4000t}\text{ mA}$

- (a) Derive an expression for the inductor voltage
- (b) Find the time where the voltage passes through zero
- (c) Derive an expression for inductor power
- (d) Find time intervals for when the inductor absorbs or delivers power

Voltage:

$$\begin{aligned}v_L(t) &= L \frac{\partial}{\partial t} i_L(t) \\v_L(t) &= 100 \times 10^{-3} \frac{\partial}{\partial t} [20e^{-2000t} - 20e^{-4000t}] \\v_L(t) &= 2000 \times 10^{-3} [-2000e^{-2000t} + 4000e^{-4000t}] \\v_L(t) &= 4000 [2e^{-4000t} - e^{-2000t}] \text{ mV} \\v_L(t) &= 4 [2e^{-4000t} - e^{-2000t}] \text{ V}\end{aligned}$$

Where does $v_L(t) = 0$?

$$\begin{aligned}2e^{-4000t} - e^{-2000t} &= 0 \\2e^{-4000t} &= e^{-2000t} \\\ln 2e^{-4000t} &= \ln e^{-2000t} \\\ln 2 + \ln e^{-4000t} &= \ln e^{-2000t} \\0.693 &= 2000t \\t &= 0.347 \text{ ms}\end{aligned}$$

Inductor Power:

$$\begin{aligned}p_L(t) &= v_L(t)i_L(t) \\p_L(t) &= 4 [2e^{-4000t} - e^{-2000t}] \times 20 \times 10^{-3} [e^{-2000t} - e^{-4000t}] \\p_L(t) &= 80 \times 10^{-3} [3e^{-6000t} - 2e^{-8000t} - e^{-4000t}] \\p_L(t) &= -80e^{-4000t} + 240e^{-6000t} - 160e^{-8000t} \text{ mW}\end{aligned}$$

Absorbing or delivering?

We know from part (b) that the zero crossing is at $t = 0.347\text{ ms}$. Let's check the sign of our power at a point above and below that cut off.

$$\begin{aligned}p_L(0.1 \text{ ms}) &= -80e^{-4000 \times 0.0001} + 240e^{-6000 \times 0.0001} - 160e^{-8000 \times 0.0001} \text{ mW} \\p_L(0.1 \text{ ms}) &= 6.19 \text{ mW}\end{aligned} \tag{32}$$

$$\begin{aligned}p_L(0.5 \text{ ms}) &= -80e^{-4000 \times 0.0005} + 240e^{-6000 \times 0.0005} - 160e^{-8000 \times 0.0005} \text{ mW} \\p_L(0.5 \text{ ms}) &= -1.81 \text{ mW}\end{aligned} \tag{33}$$

Therefore (based on the passive sign convention) power is absorbed for $t < 0.347\text{ ms}$ and delivered for $t > 0.347\text{ ms}$

SOLUTION

ECE231: Electrical Circuits and Systems I - Spring 2016 Lecture 20: Capacitors and Inductors

3 Equivalent Capacitance and Inductance

I am going to give you the equations without a derivation or proof. Please see the book for derivation.

3.1 Equivalent Capacitance

Parallel Connection

$$C_{eq} = \sum_{n=1}^k C_n \quad (34)$$

Series Connection

$$C_{eq} = \left[\sum_{n=1}^k \frac{1}{C_n} \right]^{-1} \quad (35)$$

3.2 Equivalent Inductance

Parallel Connection

$$L_{eq} = \left[\sum_{n=1}^k \frac{1}{L_n} \right]^{-1} \quad (36)$$

Series Connection

$$L_{eq} = \sum_{n=1}^k L_n \quad (37)$$

SOLUTION

ECE231: Electrical Circuits and Systems I - Spring 2016

Lecture 20: Capacitors and Inductors

4 Practical Circuits

Over the last few lessons, we have learned about Op Amps, Capacitors and Inductors. Can we build any practical circuits using these devices? Let's begin by looking at the circuit in Figure 3. Let's analyze this circuit to determine what it does.

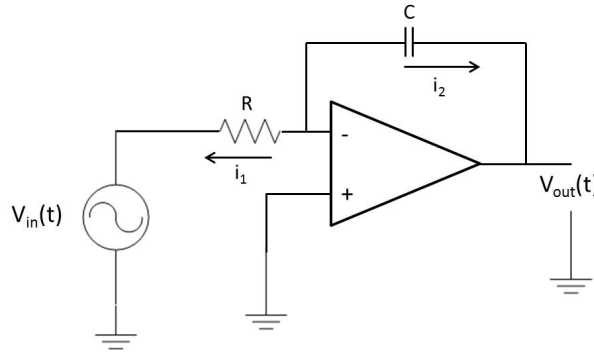


Figure 3: Integrator circuit

We can start our analysis by writing a KCL equation at the inverting node:

$$i_1(t) + i_2(t) = 0 \quad (38)$$

which can also be written as

$$-\frac{v_{in}(t)}{R} - C \frac{\partial v_{out}(t)}{\partial t} = 0 \quad (39)$$

or

$$\frac{v_{in}(t)}{R} + C \frac{\partial v_{out}(t)}{\partial t} = 0 \quad (40)$$

Next we solve for $v_{out}(t)$

$$\partial v_{out}(t) = -\frac{1}{RC} v_{in}(t) \partial t \quad (41)$$

now we can take the integral of both sides...

$$\int_0^t \partial v_{out}(t) = -\frac{1}{RC} \int_0^t v_{in}(x) \partial x \quad (42)$$

where x is a dummy variable of integration

$$v_{out}(t) = v_{out}(0) - \frac{1}{RC} \int_0^t v_{in}(x) \partial x \quad (43)$$

So this circuit integrates the input....It is an integrator!

SOLUTION

ECE231: Electrical Circuits and Systems I - Spring 2016

Lecture 20: Capacitors and Inductors

What about the circuit shown in Figure 4?

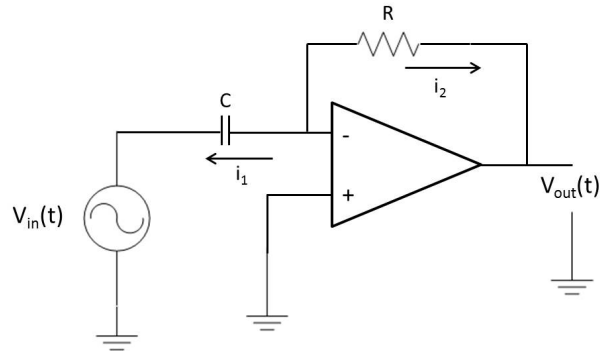


Figure 4: Differentiator circuit

We start the analysis the same way; KCL at the inverting node

$$i_1(t) + i_2(t) = 0 \quad (44)$$

which can also be written as

$$-C \frac{\partial v_{in}(t)}{\partial t} - \frac{v_{out}(t)}{R} = 0 \quad (45)$$

or

$$C \frac{\partial v_{in}(t)}{\partial t} + \frac{v_{out}(t)}{R} = 0 \quad (46)$$

Next we solve for $v_{out}(t)$

$$v_{out}(t) = -RC \frac{\partial v_{in}(t)}{\partial t} \quad (47)$$

SO THIS CIRCUIT IS A DIFFERENTIATOR!!!