



Lecture 30: Phasors Circuit Analysis and Design Part 2

OBJECTIVES:

1. Learn to apply circuit analysis techniques we already know to solve circuits in the phasor domain

READING

Required : Textbook, section 8.4–8.5, pages 402–426

Optional :

1 Introduction

Today we continue our analysis of phasor circuits. Last class we did examples of:

1. Parallel and series combinations of **Impedances**
2. Voltage and Current Division
3. Mesh and Node Analysis

Today we will look at:

1. Proportionality and Superposition
2. Thevenin and Norton equivalent circuits

All these things still apply to phasor domain circuits. As a reminder, phasor analysis only applies to the steady state sinusoidal responses. Phasor analysis does not tell you anything about the transient response.

2 Proportionality

Back in lesson 8 we introduced this idea of proportionality which states that for a linear circuit, any change to the input has a proportional change to the output. Stated mathematically:

$$y = Kx$$

where x is the input, y is the output, and K is the proportionality factor.

This also applies to phasors and can be written as:

$$\mathbf{Y} = \mathbf{KX}$$

SOLUTION

ECE231: Electrical Circuits and Systems I - Block III Lecture 30: Phasors Circuit Analysis and Design Part 2

where Y , X , and K are all in general complex.

To make use of proportionality, the book talks about the *Unit Output Method*.... I prefer the *Unit Input Method*. Let's do an example:

Example 1– This example is a modified version of textbook exercise 8-22. For the circuit shown in Figure 1, use the Unit Input Method to find \mathbf{I}_o

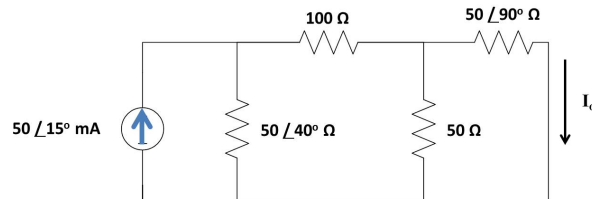


Figure 1: Circuit to accompany example 1

STEP 1 - ASSUME THE INPUT CURRENT IS 1 A & SOLVE FOR \mathbf{I}_o .

SOURCE TRANSFORM

ASSUMES 1 A INPUT CURRENT

$$V_o = 50 \angle 40^\circ \left[\frac{35 \angle 45^\circ}{35 \angle 45^\circ + 142 \angle 13^\circ} \right] = 10.13 \angle 66^\circ$$
$$\mathbf{I}_o = \frac{V_o}{50 \angle 90^\circ} = 202.7 \angle -24^\circ \text{ mA}$$

STEP 2 - MULTIPLY \mathbf{I}_o BY ORIGINAL INPUT

$$\mathbf{I}_o = (202.7 \times 10^{-3} \angle -24^\circ) (50 \angle 15^\circ)$$
$$= 10.13 \angle -9.1^\circ$$

SOLUTION

ECE231: Electrical Circuits and Systems I - Block III Lecture 30: Phasors Circuit Analysis and Design Part 2

3 Superposition

Before we jump right into an example, now is a good opportunity to remind you that phasor analysis only works for circuits that are excited by a single sinusoidal frequency. This does not mean we cannot have more than one source, it just means they all have to have the same frequency (ω).

Example 2 – Textbook Exercise 8-23 — For the circuit in Figure 2, use superposition to find I_x .

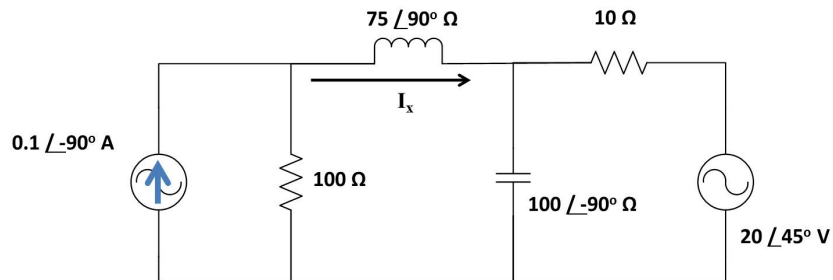


Figure 2: Circuit to accompany example 2

STEP 1 - TURN OFF VOLTAGE SOURCE & FIND I_x

$0.1 \angle -90^\circ$

$75 \angle 90^\circ$

10Ω

100Ω

$100 \angle -90^\circ$

I_1

$0.1 \angle -90^\circ$

100

$74.7 \angle 81.9^\circ$

CURRENT DIVISION $I_1 = 0.1 \angle -90^\circ \left[\frac{100}{100 + 74.7 \angle 81.9^\circ} \right] = 75.45 \angle -123.9^\circ \text{ mA}$

STEP 2 - TURN OFF CURRENT SOURCE & FIND I_x

$75 \angle 90^\circ$

10

100

$100 \angle -90^\circ$

$20 \angle 45^\circ$

I_2

$20 \angle 45^\circ$

10

$V_o = 121 \angle -39.1^\circ$

$V_o = 20 \angle 45^\circ \left[\frac{121 \angle -39.1^\circ}{10 + 121 \angle -39.1^\circ} \right] = 18.8 \angle 42^\circ$

$I_2 = \frac{-V_o}{100 + j75} = 150.2 \angle -174.7^\circ \text{ mA}$

STEP 3 - SUM CURRENTS

$I_x = I_1 + I_2 = 206 \angle -158^\circ \text{ mA}$

SOLUTION

ECE231: Electrical Circuits and Systems I - Block III Lecture 30: Phasors Circuit Analysis and Design Part 2

4 Thevenin's and Norton's Theorems

This section will offer a quick review of Thevenin's and Norton's Theorems before we work a couple of examples.

For Thevenin's theorem, we will take a *source* circuit that is connected to some *load* circuit and replace the source circuit with a single voltage source in series with a single *impedance*. To do this we must find the value of the source voltage and the *Thevenin impedance*. The source voltage is found by calculating the open circuit voltage if the load is removed. The easiest way to calculate the Thevenin Impedance is by using look-back.

Example 3– Textbook Exercise 8-29 — For the circuit in example 2 (Figure 2), find the Thevenin circuit seen by the inductor then calculate $\mathbf{I_X}$.

STEP 1 - FIND V_{oc}

USE NODE ANALYSIS $[V_{oc} = V_{AB}]$

① $V_A = (0.1 \angle -90^\circ)(100\Omega) = 10 \angle -90^\circ$

② $\frac{V_B - 20 \angle 45^\circ}{10} + \frac{V_B}{100 \angle -90^\circ} = 0$


$$V_B \left[\frac{1}{10} + \frac{1}{100 \angle -90} \right] = 2 \angle 45^\circ$$
$$V_B = 19 \angle 39.25^\circ$$
$$\therefore V_{oc} = 27.34 \angle -124.3^\circ = -15.4 - j22.6 \text{ V.}$$

STEP 2 - FIND Z_T

$$Z_T = 100 + [10 \parallel 100 \angle -90]$$
$$= 100 + \left[\frac{1000 \angle -90}{10 - j100} \right] = 109.9 - j0.982\Omega$$
$$= 109.9 \angle -0.5^\circ$$

SOLUTION

STEP 3 - DRAW THEVENIN CIRCUIT

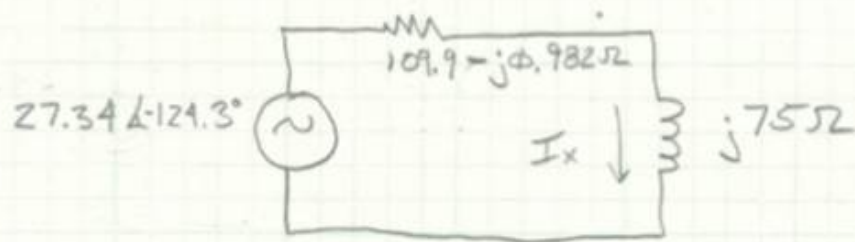

STEP 4 - SOLVE FOR I_x

$$\begin{aligned} Z_{eq} &= 109.9 - j0.982 + j75 \\ &= 109.9 + j74.018 = 132.5 \angle 34^\circ \end{aligned}$$

$$I_x = \frac{V_{oc}}{Z_{eq}} = \frac{27 \angle -124.3^\circ}{132.5 \angle 34^\circ} = 0.203 \angle -158^\circ$$

MATCHES SUPER-POSITION SOLUTION


SOLUTION

ECE231: Electrical Circuits and Systems I - Block III Lecture 30: Phasors Circuit Analysis and Design Part 2

Norton's Theorem is like Thevenin's except we find a current source in parallel with an impedance.

Example 4 – Rework Example 3 with Norton's Theorem.

STEP 1 - FIND I_{sc}

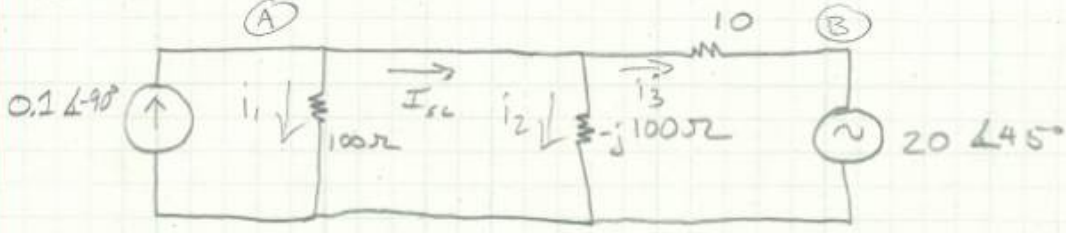


NODE ANALYSIS

$$\textcircled{A} - 0.1 \angle 90^\circ + \frac{V_A}{100} + \frac{V_A}{-j100} + \frac{V_A - 20 \angle 45^\circ}{10} = 0$$
$$V_A \left[\frac{1}{100} + \frac{1}{-j100} + \frac{1}{10} \right] = 2 \angle 45^\circ + 0.1 \angle 90^\circ$$
$$V_A = 17.5 \angle 37.7^\circ$$
$$I_{sc} = \frac{V_A}{-j100} + \frac{V_A - 20 \angle 45^\circ}{10} = 0.2488 \angle -37.7^\circ$$

SOLUTION

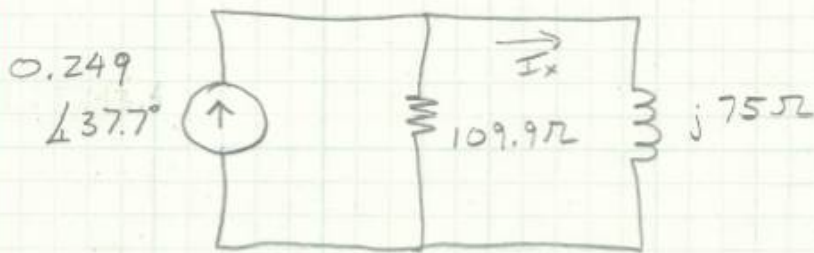STEP 2 - USING Z_T FROM EXAMPLE 3, DRAW NORTON CIRCUIT



STEP 3 - USE CURRENT DIVIDER TO FIND I_x

$$I_x = 0.249 \angle 37.7^\circ \left[\frac{109.9}{109.9 + j75 \Omega} \right]$$

$$I_x = 206 \angle -157.6 \text{ mA}$$