



## Lecture 15: Operational Amplifiers - Part 2

### OBJECTIVES:

1. Starting with the ideal Op Amp model, develop circuits for Summing and Subtracting Amplifiers

### READING

#### Required :

- Textbook, section 4.4, pages 190–201

#### Optional : None

### 1 The Summing Amplifier

Often in circuit design, we will need to add to signals together – this CANNOT be done by simply connecting two wires, although many of you in your solutions will try that method. To add two signals we must use a device called an *adder* or *summing amplifier*. In this section we will design a weighted (and inverting) summing amplifier.

#### 1.1 Derivation

Let's start by looking at the inverting Op Amp discussed in last class (see Figure ??)

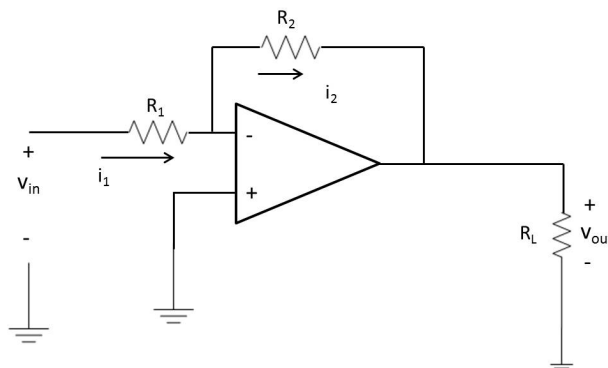


Figure 1: Inverting Op Amp

Recall that the transfer characteristic for this amplifier is:

$$\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1} \quad (1)$$

## SOLUTION

### ECE231: Electrical Circuits and Systems I - Block II Lecture 15: Operational Amplifiers - Part 2

---

which can also be written as

$$V_{out} = -\frac{V_{in}}{R_1}R_2 \quad (2)$$

but since  $\frac{V_{in}}{R_1} = i_1$  we can say the output voltage is really determined by the input current,  $i_1$ .

**Are there other ways of increasing the input current without increasing  $V_{in}$ ?** Consider the circuit shown in Figure ??

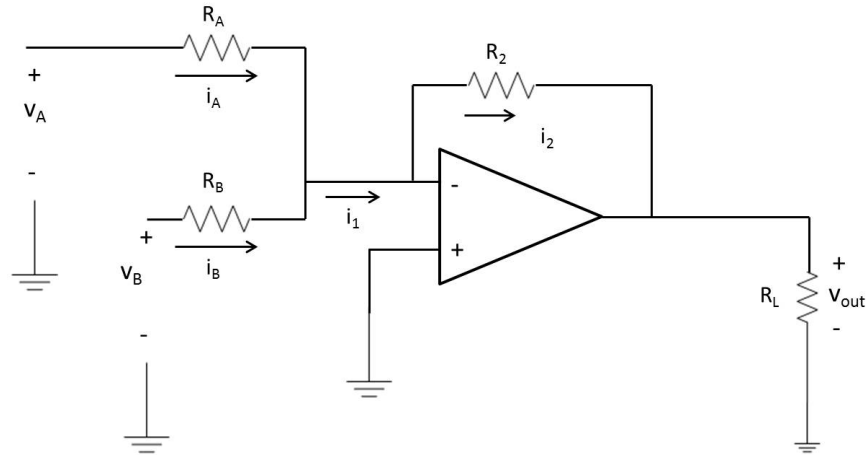


Figure 2: Inverting Summer

The output voltage is still fully determined by the input current,  $i_1$ ; but now  $i_1$  is the *sum* of two currents,  $i_A$  and  $i_B$ .

Let's derive a transfer characteristic of this amplifier circuit that relates  $V_{out}$  to  $V_A$  and  $V_B$ .

*Start by writing a KCL equation at the inverting terminal*

$$i_A + i_B = i_2 + i_n \quad (3)$$

*but we know  $i_n = 0$  so*

$$i_A + i_B = i_2 \quad (4)$$

*Since we also know that  $v_n = 0$  we can write  $i_A$  and  $i_B$  in terms of  $V_A$  and  $V_B$  and  $V_B = 0 = V_n$*

$$\frac{V_A - V_n}{R_A} + \frac{V_B - V_n}{R_B} = \frac{V_A}{R_A} + \frac{V_B}{R_B} = i_2 \quad (5)$$

*simplifying*

$$\frac{V_A}{R_A} + \frac{V_B}{R_B} = \frac{-V_{out}}{R_2} \quad (6)$$

*which solving for  $V_{out}$  gives*

$$V_{out} = -\left(\frac{R_2}{R_A}V_A + \frac{R_2}{R_B}V_B\right) \quad (7)$$

*Thus the name weighted, inverting summer*

This derivation is easily extended to an arbitrary number of inputs.

A block diagram of a summer is shown in Figure ??. It should be noted that the gains ( $K_1$  and  $K_2$ ) are typically negative in our implementation

## SOLUTION

### ECE231: Electrical Circuits and Systems I - Block II Lecture 15: Operational Amplifiers - Part 2

---

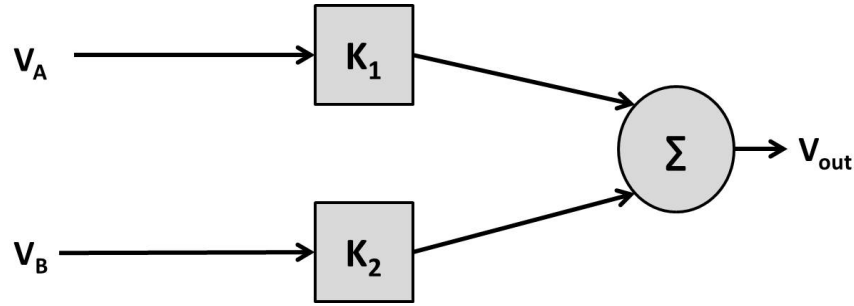


Figure 3: Summer Block Diagram

#### 1.2 Examples

**Textbook Design Example 4-16** Design an inverting summer (refer to Figure ??) that implements the following transfer characteristic:

$$V_{out} = -(5V_A + 13V_B) \quad (8)$$

*Looking back at the transfer characteristic for an inverting summer we know we need the resistances to satisfy the following relationships*

$$\frac{R_2}{R_A} = 5 \quad (9)$$

$$\frac{R_2}{R_B} = 13 \quad (10)$$

*If we limit ourselves to standard resistance values, we can start by selecting a value for  $R_2$ . Let's let  $R_2 = 91 \text{ k}\Omega$ . We can then solve for  $R_A$  and  $R_B$  and select the closest standard value. It is always good to verify that you are within about 5% of your desired gain. We select  $R_A = 18 \text{ k}\Omega$  and  $R_B = 6.8 \text{ k}\Omega$ . These values yield gains of*

$$K_1 = \frac{91 \text{ k}\Omega}{18 \text{ k}\Omega} = 5.0556 \quad (11)$$

$$K_2 = \frac{91 \text{ k}\Omega}{6.8 \text{ k}\Omega} = 13.3824 \quad (12)$$

#### Textbook Exercise 4-23

(a) For the design above find  $V_{out}$  if  $V_A = 2 \text{ V}$  and  $V_B = -0.5 \text{ V}$

(b) If  $V_A = 500 \text{ mV}$  and  $V_{CC} = 15 \text{ V}$ , what is the maximum value of  $V_B$  for linear operation?

*part (a) is just plug and chug*

$$V_{out} = -(K_1V_A + K_2V_B) = -(5.05 \times 2 \text{ V} + 13.38 \times (-0.5)) = -3.41 \text{ V} \quad (13)$$

*for part (b) we know  $|V_{out}| \leq 15 \text{ V}$ . If we set  $V_{out} = 15 \text{ V}$  in the transfer characteristic equation and solve for  $V_B$  we get:*

$$V_B = -\frac{V_{out} + K_1V_A}{K_2} = -\frac{15 \text{ V} + 5.05 \times 500 \text{ mV}}{13.38} = -1.31 \text{ V} \quad (14)$$

*If we set  $V_{out} = -15 \text{ V}$  in the transfer characteristic equation and solve for  $V_B$  we get:*

$$V_B = -\frac{V_{out} + K_1V_A}{K_2} = -\frac{-15 \text{ V} + 5.05 \times 500 \text{ mV}}{13.38} = 932 \text{ mV} \quad (15)$$

*After checking both edges, pick the largest. Intuition may have allowed you to select the largest without doing both calculations.*

## SOLUTION

### ECE231: Electrical Circuits and Systems I - Block II Lecture 15: Operational Amplifiers - Part 2

---

## 2 The Differential Amplifier or Subtractor

To understand the differential amplifier, let's start with the block diagram shown in Figure ???. Notice this block diagram is very similar to the summer block diagram, except that one of the inputs is into an *inverting terminal*.

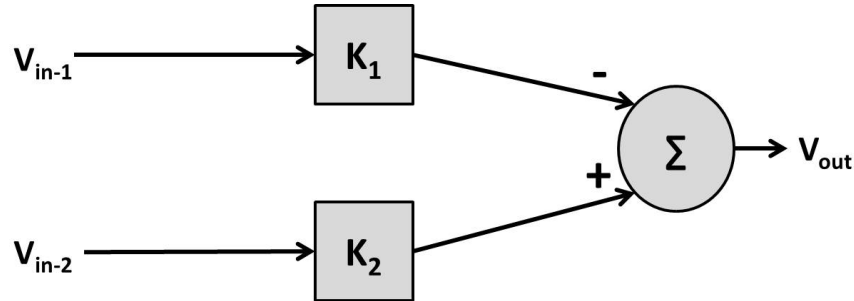


Figure 4: Differential Amplifier Block Diagram

### 2.1 Derivation

Rather than try to design a differential amplifier, I will give you the circuit (see Figure ??) and then we can derive the transfer characteristic.

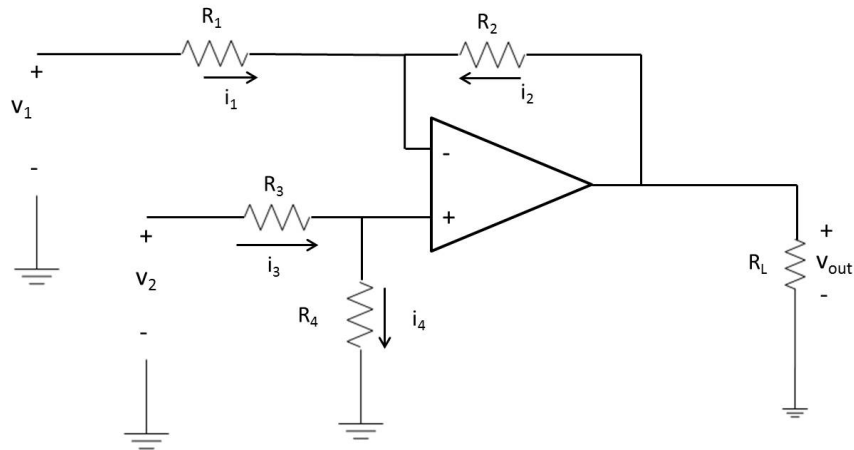


Figure 5: Differential Amplifier Circuit Diagram

The derivation below will take advantage of the *Superposition* principle.


## SOLUTION

### ECE231: Electrical Circuits and Systems I - Block II Lecture 15: Operational Amplifiers - Part 2


---

We will start by *turning off*  $V_2$  (remember to turn off a voltage source you short it) and finding the output resulting from  $V_1$ .

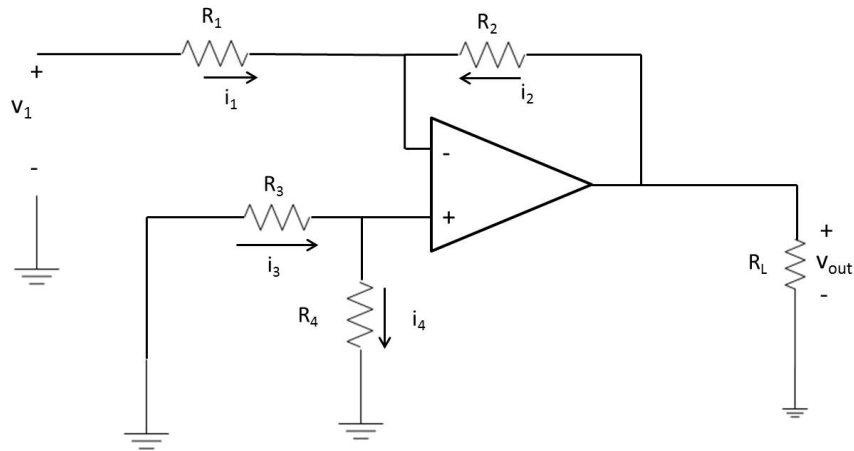*With  $V_2$  turned off the circuit becomes:*



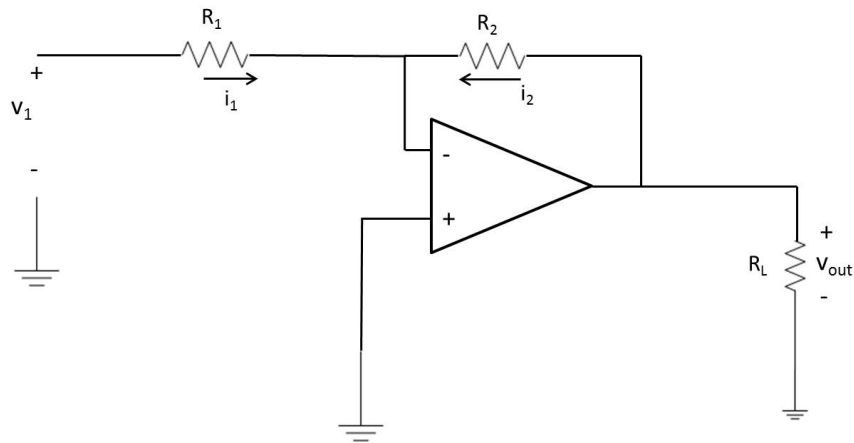*With  $V_2$  off  $i_3$  and  $i_4$  are zero and the circuit becomes which is easily recognized as an inverting amplifier.*



*The transfer characteristic is*


$$V_{out-1} = -\frac{R_2}{R_1} V_1 \quad (16)$$

## SOLUTION
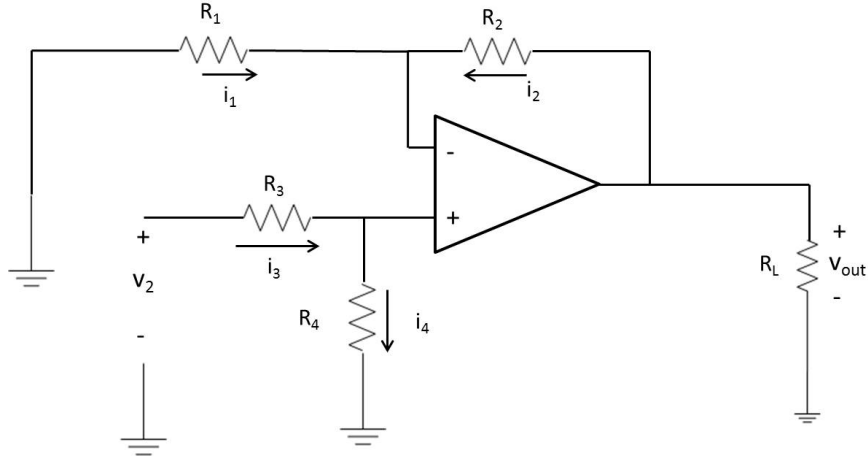
### ECE231: Electrical Circuits and Systems I - Block II Lecture 15: Operational Amplifiers - Part 2

---

Continuing the derivation we now *turn off*  $V_1$ . The circuit would now look like



We now can find the voltage at the non-inverting terminal,  $v_p$  using voltage division

$$v_p = \frac{R_4}{R_3 + R_4} V_2 \quad (17)$$

and we know that  $v_p = v_n$  therefore

$$v_n = \frac{R_4}{R_3 + R_4} V_2 \quad (18)$$

Now do a voltage divider

$$V_{out-2} = \frac{R_1 + R_2}{R_1} V_n \quad (19)$$

$$V_{out-2} = \frac{R_1 + R_2}{R_1} \frac{R_4}{R_3 + R_4} V_2 \quad (20)$$

$$(21)$$

Now that we have the output from  $V_1$  and  $V_2$  we can add them

$$V_{out} = V_{out-1} + V_{out-2} = K_1 V_{out-1} + K_2 V_{out-2} \quad (22)$$

$$V_{out} = -\frac{R_2}{R_1} V_1 + \left[ \frac{R_4}{R_3 + R_4} \right] \left[ \frac{R_1 + R_2}{R_1} \right] V_2 \quad (23)$$

so referring back to the block diagram

$$K_1 = \frac{R_2}{R_1} \quad (24)$$

$$K_2 = \left[ \frac{R_4}{R_3 + R_4} \right] \left[ \frac{R_1 + R_2}{R_1} \right] \quad (25)$$

*Note: We dropped the negatives sign because it is accounted for in the block diagram at the summing junction*

## SOLUTION

### ECE231: Electrical Circuits and Systems I - Block II Lecture 15: Operational Amplifiers - Part 2

---

#### 2.2 Examples

##### Textbook Exercise 4-25

(a) Find the transfer characteristic of a differential amplifier if:  $R_1 = 10 \text{ k}\Omega$ ,  $R_2 = 40 \text{ k}\Omega$ ,  $R_3 = 10 \text{ k}\Omega$ , and  $R_4 = 15 \text{ k}\Omega$ .

(b) If  $V_{CC} = \pm 15 \text{ V}$  and  $V_1 = 3 \text{ V}$  what is the allowable range of  $V_2$  for linear operation?

*part (a) is plug and chug.... The transfer characteristic written in terms of gains,  $K_1$  and  $K_2$  is :*

$$V_{out} = -K_1 V_1 + K_2 V_2 \quad (26)$$

*solve for gains,  $K_1$  and  $K_2$*

$$K_1 = \frac{40 \text{ k}\Omega}{10 \text{ k}\Omega} = 4 \quad (27)$$

$$K_2 = \left[ \frac{15 \text{ k}\Omega}{10 \text{ k}\Omega + 15 \text{ k}\Omega} \right] \left[ \frac{10 \text{ k}\Omega + 40 \text{ k}\Omega}{10 \text{ k}\Omega} \right] = 3 \quad (28)$$

*Plugging these gains into the transfer characteristic gives*

$$V_{out} = -4V_1 + 3V_2 \quad (29)$$

*For part (b) we start by solving the transfer characteristic for  $V_2$*

$$V_2 = \frac{V_{out} + 4V_1}{3} \quad (30)$$

*we now solve for the two cases: (1)  $V_{out} = 15 \text{ V}$ , (2)  $V_{out} = -15 \text{ V}$*

$$V_2 = \frac{-15 + (4 \times 3 \text{ V})}{3} = -1 \text{ V} \quad (31)$$

$$V_2 = \frac{15 + (4 \times 3 \text{ V})}{3} = 9 \text{ V} \quad (32)$$

*therefore*

$$-1 \text{ V} \leq V_2 \leq 9 \text{ V} \quad (33)$$