

## Lecture 10: Maximum Power Transfer

### OBJECTIVES:

1. Derive and understand the conditions for Maximum Power Transfer

### READING

#### Required :

- Textbook, sections 3.5, pages 122–125

#### Optional : None

### 1 Maximum Power Transfer

As discussed in last lesson, an interface is a connection between two circuits where a signal level can be observed, measured or specified. But what is the maximum signal level that can be transferred across an interface? That is what we will explore this lesson. For the purposes of this discussion, we will only consider examples where both the source circuit and the load circuit are linear resistive circuits; see Figure 1.

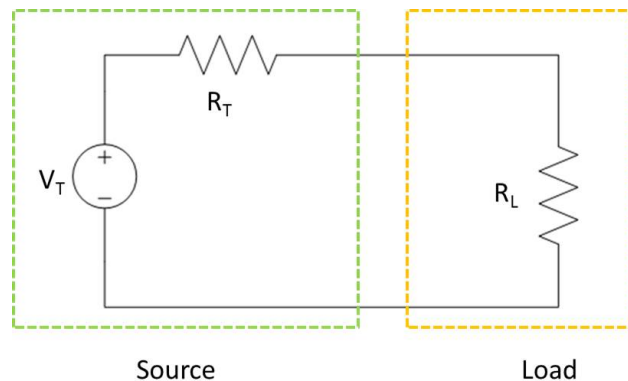


Figure 1: Circuit showing linear source and load

**What do we mean by maximum power transfer?**

*This is the condition when the power consumed by the load is at its maximum.*

## SOLUTION

ECE231: Electrical Circuits and Systems I - Fall 2016

### Lecture 10: Maximum Power Transfer

---

**What are the conditions for maximum power transfer?**

Assume in this discussion that we cannot control  $R_T$ . This entire discussion will reference Figure 1

Start by writing an equation for the voltage across the load resistor:

$$v_{Load} = \frac{R_L}{R_L + R_T} V_T \quad (1)$$

*You should be able to easily recognize that  $v_{Load}$  gets larger as  $R_L$  gets larger; if  $R_L = \infty$  then  $v_{Load} = V_T$  which is the max value it can take on.*

Next, let's find the current in the loop:

$$i_{Load} = \frac{V_T}{R_L + R_T} \quad (2)$$

*It should be easy to see that  $i_{Load}$  grows as  $R_L$  get smaller. If  $R_L = 0$  this  $i_{Load} = i_{sc} = \frac{V_T}{R_T}$*

But

$$P_{Load} = v_{Load} i_{Load} \quad (3)$$

which, using previous equations, is:

$$P_{Load} = \frac{R_L}{R_L + R_T} V_T \frac{V_T}{R_L + R_T} \quad (4)$$

$$P_{Load} = \frac{R_L V_T^2}{(R_L + R_T)^2} \quad (5)$$

**How can we maximize this equation?**

*Take the derivative (with respect to  $R_L$ ) and set it equal to zero!*

*To take this derivative we need to use the quotient rule:*

*If*

$$f(x) = \frac{g(x)}{h(x)} \quad (6)$$

*then*

$$\frac{\partial f(x)}{\partial x} = \frac{h(x) \partial g(x) - g(x) \partial h(x)}{h^2(x)} \quad (7)$$

*So,*

$$\frac{\partial P}{\partial R_L} = \frac{(R_L + R_T)^2 V_T^2 - 2 R_L V_T^2 (R_L + R_T)}{(R_L + R_T)^4} \quad (8)$$

*which will simplify to*

$$\frac{\partial P}{\partial R_L} = V_T^2 \frac{R_T - R_L}{(R_L + R_T)^3} \quad (9)$$

*If we set that equal to zero*

$$V_T^2 \frac{R_T - R_L}{(R_L + R_T)^3} = 0 \quad (10)$$

*Then solve for  $R_L$*

$$R_L = R_T \quad (11)$$

## SOLUTION

ECE231: Electrical Circuits and Systems I - Fall 2016

### Lecture 10: Maximum Power Transfer

---

Now found the value for  $R_T$  that give max power, what is the maximum power delivered?

*Plug  $R_L = R_T$  into the power equation and solve to get*

$$P_{Load} = \frac{R_T V_T^2}{(2R_L)^2} = \frac{R_T V_T^2}{4R_T^2} = \frac{V_T^2}{4R_T} = P_{MAX} \quad (12)$$

$$P_{MAX} = \frac{V_T^2}{4R_T} = \frac{V_T i_N}{4} = \frac{i_N^2 R_T}{4} \quad (13)$$

Note,  $P_{MAX}$  does not imply maximum efficiency too (see book p. 117 for more details).

## 2 Examples

### 2.1 Example 1 - Textbook Exercise 3-33


A source circuit delivers 4 V to a  $50\Omega$  load and 5 V to a  $75\Omega$  load. Find the maximum voltage, current, and power available from the source.

## SOLUTION

ECE231: Electrical Circuits and Systems I - Fall 2016

### Lecture 10: Maximum Power Transfer

---

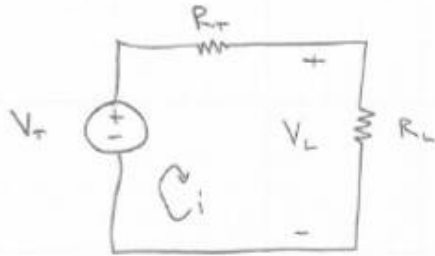

$$i = \frac{V_L}{R_L}$$

KVL

$$V_T - iR_T - V_L = 0$$

$$\textcircled{1} \quad V_T - \frac{4}{50} R_T - 4 = 0$$

$$\textcircled{2} \quad V_T - \frac{5}{75} R_T - 5 = 0$$

$$\begin{bmatrix} 1 & -0.08 \\ 1 & -0.067 \end{bmatrix} \begin{bmatrix} V_T \\ R_T \end{bmatrix} = \begin{bmatrix} 4 \\ 5 \end{bmatrix}$$

$$V_T = 10.15 \text{ V}$$

$$R_T = 77 \Omega$$

$$\text{MAX VOLTAGE} = V_{oc} = 10.15 \text{ V}$$

$$\text{MAX CURRENT} = i_{sc} = \frac{V_{oc}}{R_T} = 0.131 = 131 \mu\text{A}$$

$$\text{MAX POWER} = \frac{(10.15)^2}{4 \cdot 77} = 0.334 \text{ W}$$

## SOLUTION

ECE231: Electrical Circuits and Systems I - Fall 2016

### Lecture 10: Maximum Power Transfer

#### 2.2 Example 2

For the circuit shown in Figure 2, find the value of  $R_L$  that gives maximum power transfer and find the maximum amount of power absorbed by  $R_L$ .


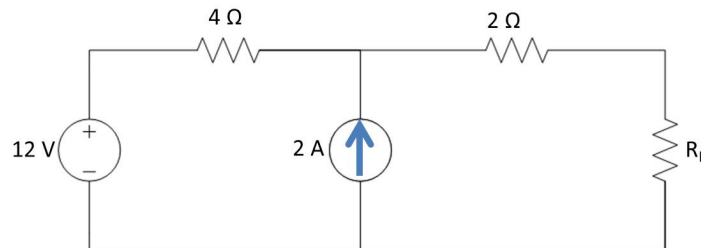


Figure 2: Example 2 Circuit

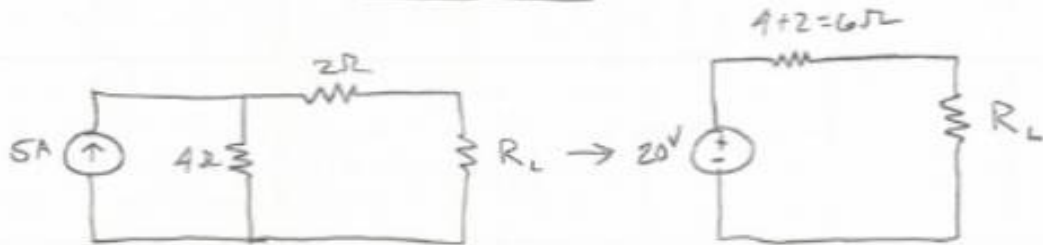- USE SOURCE TRANSFORMATION TO SIMPLIFY THE CIRCUIT



$R_L$  FOR MAXIMUM POWER TRANSFER  $= R_T$

$$R_L = 6\Omega$$

$$P_{\text{MAX}} = \frac{(20\text{V})^2}{4 R_T} = 16.7 \text{ W}$$

## SOLUTION

ECE231: Electrical Circuits and Systems I - Fall 2016

### Lecture 10: Maximum Power Transfer

#### 2.3 Example 3

For the circuit shown in Figure 3, find the value of  $R_L$  that gives maximum power transfer and find the maximum amount of power absorbed by  $R_L$ .

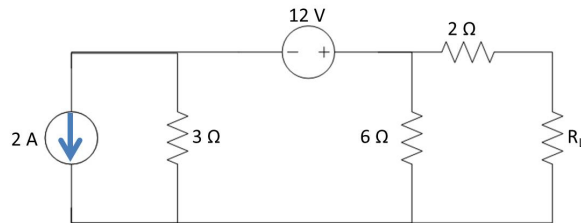


Figure 3: Example 3 Circuit

USE SOURCE TRANSFORM TO SIMPLIFY THE CIRCUIT

- FIND  $V_{OC}$

$$V_{OC} = \frac{6}{9}(6) = 4V$$

- FIND  $R_T$  USING LOOK BACK

$$R_T = (3 \parallel 6) + 2 = 4\Omega$$

$R_L = 4\Omega$

$$P_{MAX} = \frac{(4)^2}{4 \cdot 4} = 1W$$