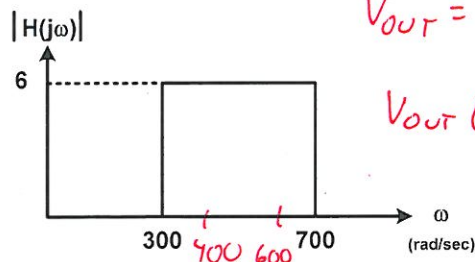


## ECE 231 Quiz 6B (Fall 2016)

NAME: \_\_\_\_\_

*Chess-key*


\_\_\_\_\_/33 = \_\_\_\_ %

**Problem 1: (1pt each)** Please answer true or falseTRUE ☒ FALSE a. The cutoff frequency of the high-pass filter must be <sup>below</sup> above the cutoff frequency of the low-pass filter to create a band-pass filter by cascading the filtersTRUE ☒ FALSE b. Given  $|H|_{dB} = 20 \log_{10} |H|_{abs}$  and that  $|H|_{dB}$  (gain in decibel) is a large negative number, this then means that  $|H|_{abs}$  (gain in absolute) is a very small positive numberTRUE ☒ FALSE c. The cutoff frequencies for a band-pass filter will only correspond to the cutoff frequencies of cascaded low-pass and high-pass filters if those frequencies are sufficiently far apart**Problem 2: (4pts)** Given the "ideal" BP filter below and the following input voltage expression, $v_{in}(t) = 2V \cos(200t + 20^\circ) + 4V \cos(400t + 40^\circ) + 6V \cos(600t)$ , determine the filter output expression $v_{out}(t)$ 

$$V_{out} = 4V \times 6 \cos(400t + 40^\circ) + 6V \times 6 \cos(600t)$$

$$V_{out}(t) = 24V \cos(400t + 40^\circ) + 36V \cos(600t)$$

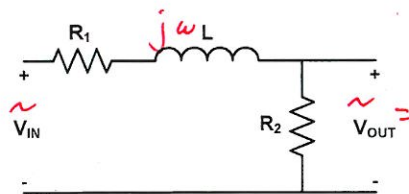**Problem 3: (7pts)** Given the following time-domain circuit, derive the transfer function and then evaluate the peak passband gain ( $K$ ) and cutoff frequency ( $\omega_c$ ) provided that  $R_1 = 400\Omega$ ,  $R_2 = 600\Omega$ ,  $L = 20mH$



$$\tilde{V}_{in} \rightarrow H(j\omega) = \frac{\tilde{V}_{out}}{\tilde{V}_{in}} = \frac{R_2}{R_1 + R_2 + j\omega L} \times \frac{\frac{1}{R_1 + R_2}}{\frac{1}{R_1 + R_2}}$$


$$H(j\omega) = \frac{R_2}{R_1 + R_2} \frac{1}{1 + j\omega \frac{L}{R_1 + R_2}} \sim \frac{K}{j\frac{\omega}{\omega_c} + 1}$$

$$\rightarrow \omega_c = \frac{R_1 + R_2}{L} = \frac{400 + 600}{.02} = 50 \text{ krad/s}$$

$$K = \frac{R_2}{R_1 + R_2} = \frac{600}{400 + 600} = 0.6$$

**Problem 4: (13pts)** Given the following circuit in the time domain

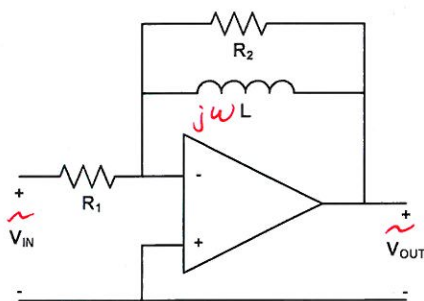a. (7pts) Derive the transfer function and determine whether this is low-pass or high-pass filter



$$\begin{aligned}
 H &= \frac{\tilde{V}_{OUT}}{\tilde{V}_{IN}} = -\frac{Z_F}{Z_i} = -\frac{(R_2 \parallel j\omega L)}{R_1} \\
 &= \left( \frac{-R_2 \times j\omega L}{R_2 + j\omega L} \right) / R_1 \times \frac{1/R_2}{1/R_2} \\
 &= \frac{-j\omega L/R_1}{1 + j\omega L/R_2} \rightarrow \underline{\text{highpass}}
 \end{aligned}$$

b. (6pts) If  $R_2 = 80k\Omega$ , find  $L$  and  $R_1$  so that the peak passband gain ( $|K|$ ) is 10 and the cutoff frequency ( $\omega_c$ ) is 4,000rad/s

$$\begin{aligned}
 \rightarrow \omega_c &= \frac{R_2}{L} \\
 L &= \frac{80K}{4K} = \boxed{20H} \\
 K j\omega \frac{L}{R_2} &= -j\omega \frac{L}{R_1} \\
 \rightarrow K &= -\frac{R_2}{R_1} \\
 |K| &= \frac{80K}{R_1} = 10 \rightarrow \boxed{R_1 = 8K\Omega}
 \end{aligned}$$

**Problem 5: (6pts)** Given the following transfer function for a real filter:  $H(j\omega) = \frac{j20\omega}{j\omega + 200}$ , if the input

to this filter is  $v_{in}(t) = 6V \cos(200t + 30^\circ)$ , find the magnitude scaling and phase shift that this filter provides and then write the expression for  $v_{out}(t)$

$$H(j200) = \frac{j20(200)}{j(200) + 200} = \frac{j4000}{j200 + 200} \stackrel{\text{calculator}}{=} \boxed{14.142 \angle 45^\circ}$$

$$V_{OUT}(t) = 6V \times 14.142 \cos(200t + 30^\circ + 45^\circ)$$

$$\boxed{V_{OUT}(t) = 84.852V \cos(200t + 75^\circ)}$$