

Lecture 3: Equivalent Resistance,  $R_{eq}$ 

## OBJECTIVES:

1. Understand *Series* and *Parallel* connections
2. Demonstrate the ability to simplify (reduce) circuits by combining resistances

## READING

## Required :

- Textbook, sections 2.3–2.4, pages 26–43

## Optional : None

## 1 Series and Parallel Combinations

## 1.1 Series

What does it mean for circuit devices to be in *series*?

1. If **two** and **only two** components share a common node, then those components are in series.
2. If the same current flows through two devices, then those components are in series. By the **same current**, I truly mean the same; not just equal. I mean the same electrons are moving through each device.

In Figure 1, resistors  $R_1$  and  $R_2$  are in series. Notice that the same current flows through both. Also notice they have one common node and no other devices share that node. Both of our definitions of series components are satisfied.

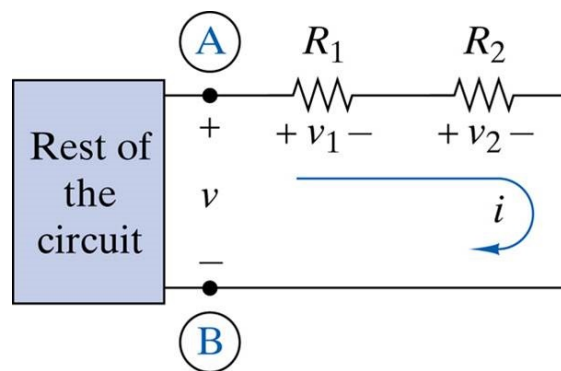


Figure 1: Series Resistors

## 1.2 Parallel

What does it mean when we say devices are in parallel?

1. If **two** and **or more** components share two common nodes, then those components are in parallel.
2. If two devices are connected to form a loop that contains only those two device, they are in parallel.
3. Parallel devices will all have the same voltage across them.

## SOLUTION

ECE231: Electrical Circuits and Systems I - Fall 2016

### Lecture 3: Equivalent Resistance, $R_{eq}$

---

*In Figure 2, devices 1, 2, and 3 are all in parallel. Notice that when taken pair-wise, you can form a loop with contains only 1 and 2, only 2 and 3, or only 1 and 3. Also you can see that all three device share two common nodes. Last, it should be obvious that the voltage across all three devices is identical.*

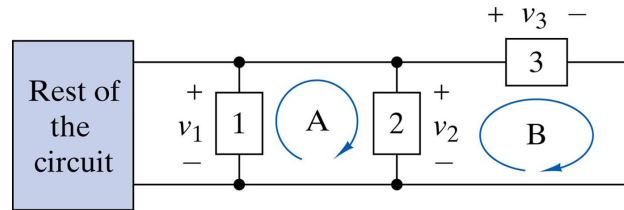


Figure 2: Parallel Resistors

## 2 Equivalent Circuits

In this section we will discuss how to simplify circuits by combining resistors into equivalent resistance values and doing source transformation.

**Equivalent Circuits** are circuits that have identical voltage-current relationships at a given pair of terminals

### 2.1 Equivalent Resistance, $R_{eq}$

The first step in being able to analyze equivalent circuits is to be able to combine resistors into a total (or equivalent) resistance. The method for combining parallel and series resistors is different and we will derive both here. An analogy for this idea of equivalent circuits is money: \$1 is equal to 4 quarters. They are the same amount of money, just comprised of different components.

#### 2.1.1 Series $R_{eq}$

To derive an equation for equivalent resistance in series circuits, let's look at the circuit shown in Figure 1. We can write a KVL equation for this circuit:

$$v_{AB} - v_1 - v_2 = 0 \quad (1)$$

We can define currents going into resistors  $R_1$  and  $R_2$  as  $i_1$  and  $i_2$  respectively. Because of the Passive Sign Convention, the currents flow into the positive nodes of the resistors. Using that we can rewrite the KVL equation as

$$v_{AB} - i_1 R_1 - i_2 R_2 = 0 \quad (2)$$

By examining the circuit (and from our definition of series resistors) we should see that  $i_1 = i_2 = i$ . So again we can rewrite the KVL equation:

$$\begin{aligned} v_{AB} - i R_1 - i R_2 &= 0 \\ v_{AB} - i(R_1 + R_2) &= 0 \end{aligned} \quad (3)$$

This final equation shows us that the series resistors can be modeled as a single resistor with an equivalent resistance of  $R_1 + R_2$ . This allows us to redraw the circuit in Figure 1 to a circuit with a single resistor; this new circuit is shown in Figure 3.

## SOLUTION

ECE231: Electrical Circuits and Systems I - Fall 2016

### Lecture 3: Equivalent Resistance, $R_{eq}$

---

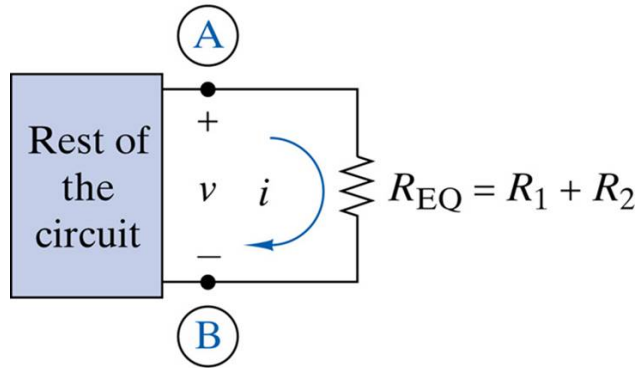


Figure 3: Series Equivalent Resistance

So, for  $k$  resistors in series:

$$R_{eq} = \sum_{n=1}^k R_n \quad (4)$$

$R_{eq}$  is always larger than any individual *series* resistor value.

#### 2.1.2 Parallel $R_{eq}$

Before we derive the equation for parallel  $R_{eq}$  we need to introduce the concept of conductance. Conductance ( $G$ ) is simply the inverse of resistance:

$$G = \frac{1}{R} \quad (5)$$

We can now rewrite Ohm's law in terms of conductances:

$$i = vG \quad (6)$$

Now that we have defined conductance, we can set off on deriving the equation for parallel equivalent resistance.

We start by examining the circuit shown in Figure 4(a). We can apply KCL at node A:

$$i = i_1 + i_2 \quad (7)$$

We can now use Ohm's law (in terms of conductance) to replace all the currents above:

$$vG_{eq} = vG_1 + vG_2 \quad (8)$$

where  $G_{eq}$  is the circuit's equivalent conductance. We can now factor and cancel the voltage ( $v$ ), which gives:

$$G_{eq} = G_1 + G_2 \quad (9)$$

But based on our definition of conductance, we have

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \quad (10)$$

This easily extends to any number of parallel resistors:

$$\frac{1}{R_{eq}} = \sum_{n=1}^k \frac{1}{R_n} \quad (11)$$

## SOLUTION

ECE231: Electrical Circuits and Systems I - Fall 2016

### Lecture 3: Equivalent Resistance, $R_{eq}$

---

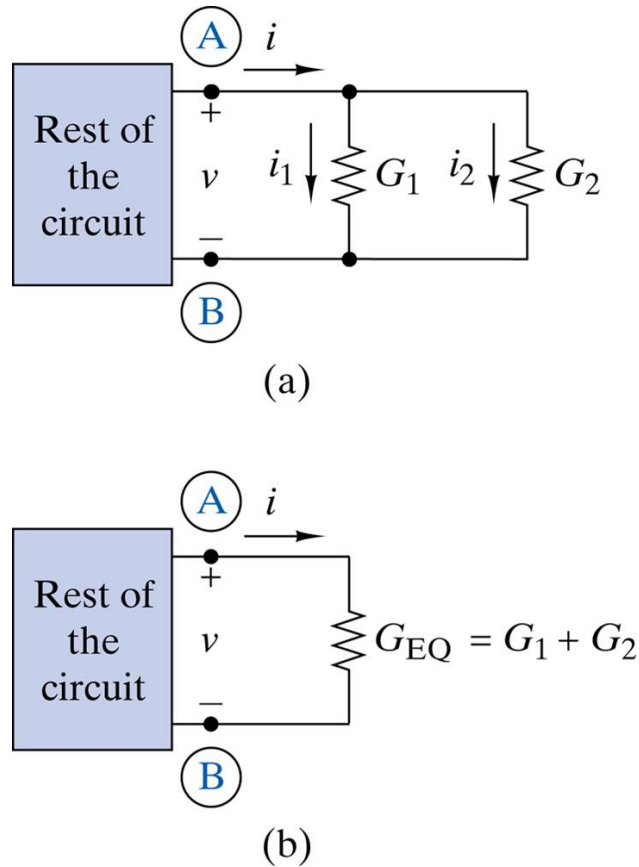


Figure 4: (a) Circuit with two parallel resistors (b) Same circuit with one equivalent resistance

$R_{eq}$  is always smaller than any individual *parallel* resistor value.

**Cool Shortcut for 2 resistor case....**

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} \quad (12)$$

If both resistors are equal resistance values, then this simplifies to

$$R_{eq} = \frac{R}{2} \quad (13)$$

## SOLUTION

ECE231: Electrical Circuits and Systems I - Fall 2016

### Lecture 3: Equivalent Resistance, $R_{eq}$

#### 2.1.3 Examples

##### Textbook Exercise 2-15 (p.39)

Find the equivalent resistance between terminals A-C, B-D, A-D, & B-C in Figure 5

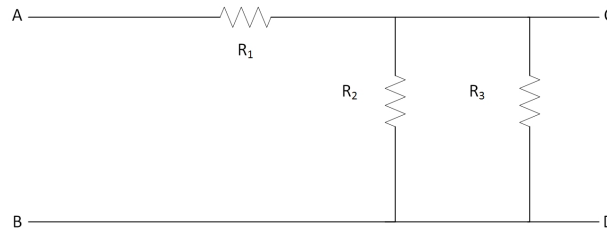


Figure 5: Circuit for text book exercise 2-15

**A-C**  
ONLY  $R_1$  IS CONNECTED BETWEEN A & C  $\therefore R_{eq} = R_1$

**B-D**  
THERE IS A SHORT CIRCUIT BETWEEN B & D  $\therefore R_{eq} = 0\Omega$

**A-D**  
  
FIRST COMBINE  $R_2 \parallel R_3$   
  
THAT COMBINATION IS IN SERIES WITH  $R_1$   
 $\therefore R_{eq} = R_1 + R_2 \parallel R_3$

**B-C**  
  
 $R_{eq} = R_2 \parallel R_3$

## SOLUTION

ECE231: Electrical Circuits and Systems I - Fall 2016

### Lecture 3: Equivalent Resistance, $R_{eq}$

---

#### Textbook Exercise 2-16 (p.39)

Find the equivalent resistance between terminals A-B, A-C, A-D, B-C, B-D, & C-D in Figure 6

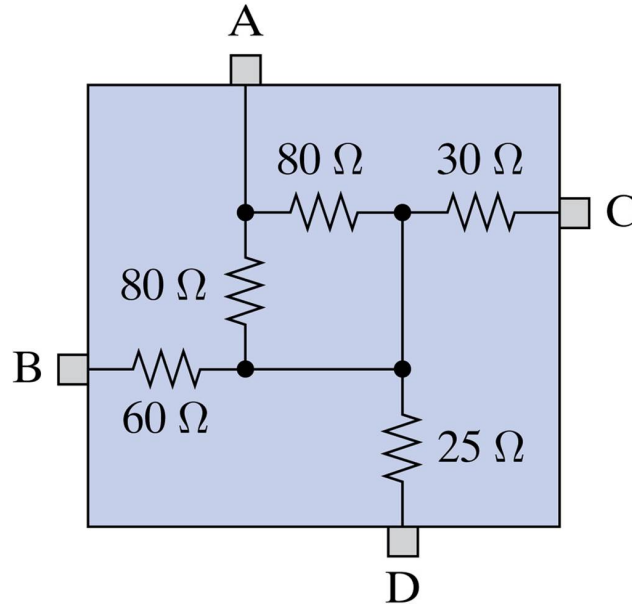


Figure 6: Circuit for text book exercise 2-16

$$AB = 80 \parallel 80 + 60$$

$$AC = 80 \parallel 80 + 30$$

$$AD = 80 \parallel 80 + 25$$

$$BC = 60 + 80 + 80 + 30$$

$$BD = 60 + 25$$


$$CD = 30 + 25$$

## SOLUTION

ECE231: Electrical Circuits and Systems I - Fall 2016

### Lecture 3: Equivalent Resistance, $R_{eq}$

A-B

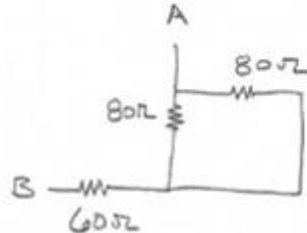

- SINCE BOTH 80Ω RESISTORS SHARE 2 NODES, THEY ARE PARALLEL

$$R_{eq} = 40\Omega$$



- NOTICE THE 60Ω & 40Ω RESISTORS SHARE ONE NODE & NO OTHER DEVICES SHARE THAT NODE,  
 $\therefore$  THEY ARE IN SERIES


$$R_{A-B} = 60\Omega + 40\Omega = 100\Omega$$

A-C



$$\begin{aligned} R_{A-C} &= 30\Omega + 80\Omega \parallel 80\Omega \\ &= 30\Omega + 40\Omega \\ &= 70\Omega \end{aligned}$$

A-D

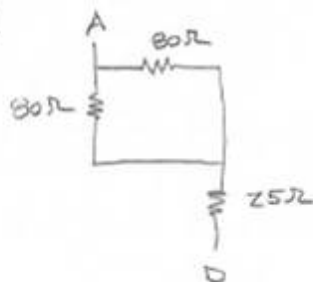


$$\begin{aligned} R_{A-D} &= 25\Omega + 80\Omega \parallel 80\Omega \\ &= 65\Omega \end{aligned}$$

## SOLUTION

ECE231: Electrical Circuits and Systems I - Fall 2016

### Lecture 3: Equivalent Resistance, $R_{eq}$


B-C

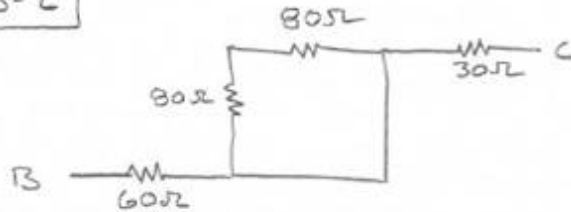

COMBINE 80Ω + 30Ω  
IN SERIES





NOTICE WE NOW  
HAVE 160Ω || 0Ω  
THIS EQUALS 0Ω

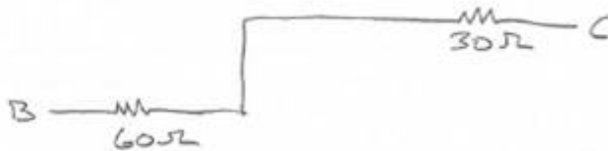

$$R_{B-C} = 60\Omega + 30\Omega = 90\Omega$$

B-D

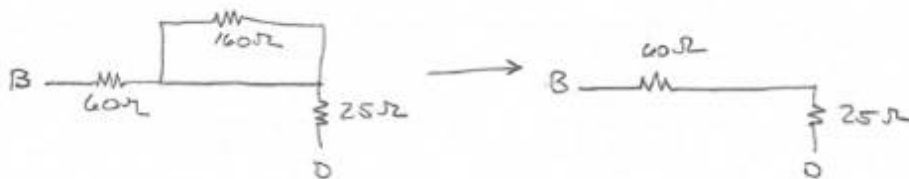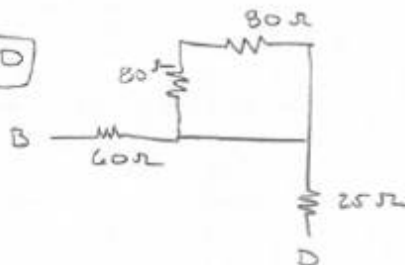

$$R_{B-D} = 85\Omega$$

C-D - LIKE 2 ABOVE

$$R_{C-D} = 55\Omega$$



## SOLUTION

ECE231: Electrical Circuits and Systems I - Fall 2016

### Lecture 3: Equivalent Resistance, $R_{eq}$

---

#### 3 Review Questions

1. When resistors are in parallel,  $R_{eq}$  is bigger or smaller than the individual component resistances?

*Smaller*

2. What does  $G$  represent?

*Conductance,  $\frac{1}{R}$*

3. How do you know if resistors are in series?

*They share only one common node and no other devices share that node. All the current from one device flows into the second device.*

4. True or False.... Resistors in series have the same voltage drop across them.

*True*