



Lecture 6: Node Voltage Analysis

OBJECTIVES:

1. Demonstrate the ability to write node voltage equations for a given circuit
2. Demonstrate the ability to solve for unknown circuit parameters using node voltage analysis

READING

Required :

- Textbook, section 3.1, pages 73-91

Optional : None

1 What is Node Voltage Analysis?

Relying on element constraints (e.g., component i-v relationships) and connection constraints (e.g., KVL and KCL) to solve complex circuits can lead to unwieldy numbers of equations. Instead we can write equations for *Node Voltages*. This is referred to as node voltage analysis. We start by learning the steps for writing node voltage equations and then looking at methods to solve those equations.

2 Circuits with NO VOLTAGE source

Without justification I will offer that node voltage analysis is easier when no voltage sources are in the circuit. These circuits contain only current sources and resistors. We will start by looking at these types of circuits.

2.1 How do we write Node Voltage equations?

Below are the steps for writing node voltage equations:

- 1. Identify a **reference node**. You will not write an equation for this node, but the voltages at the other nodes will use this as a reference.*
- 2. Write **KCL equations** at the other $N - 1$ nodes*
- 3. Write the currents in the KCL equations in terms of **node voltages** and resistances*
- 4. Rearrange the equations above into **standard form***

SOLUTION

ECE231: Electrical Circuits and Systems I - Fall 2016

Lecture 6: Node Voltage Analysis

2.2 Examples

Textbook Exercise 3–4 Formulate node voltage equations for the circuit in Figure 1 and place the results in matrix form ($\mathbf{Ax} = \mathbf{b}$)

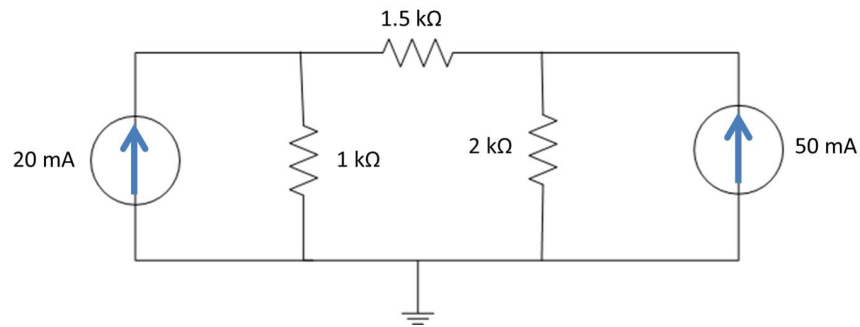



Figure 1: Circuit for textbook exercise 3–4

STEP 1

- BOTTOM NODE IS ALREADY LABELED AS REFERENCE NODE

STEP 2

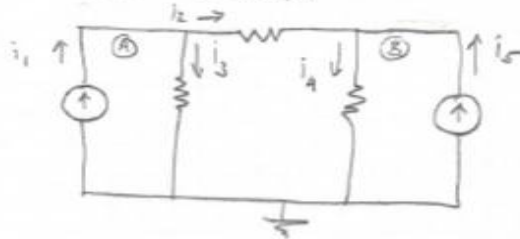- LABEL CURRENTS & WRITE KCL EQNS. FOR TOP 2 NODES.



Ⓐ $i_2 + i_3 = i_1$

Ⓑ $i_2 + i_5 = i_4$

SOLUTION

ECE231: Electrical Circuits and Systems I - Fall 2016

Lecture 6: Node Voltage Analysis

STEP 3

- PLUG IN KNOWN CURRENTS & REWRITE UNKNOWN CURRENTS IN TERMS OF VOLTAGES & RESISTANCE

$$i_1 = 20 \text{ mA}$$

$$i_5 = 50 \text{ mA}$$

$$i_2 = \frac{V_A - V_B}{1.5 \text{ k}\Omega}$$

$$i_3 = \frac{V_A}{1 \text{ k}\Omega}$$

$$i_4 = \frac{V_B}{2 \text{ k}\Omega}$$

$$\frac{V_A - V_B}{1.5 \text{ k}\Omega} + \frac{V_A}{1 \text{ k}\Omega} = 20 \text{ mA}$$

$$\frac{V_A - V_B}{1.5 \text{ k}\Omega} + 50 \text{ mA} = \frac{V_B}{2 \text{ k}\Omega}$$

STEP 4

WRITE EQUATION IN MATRIX FORM

$$\left[\frac{1}{1.5 \text{ k}\Omega} + \frac{1}{1 \text{ k}\Omega} \right] V_A - \frac{1}{1.5 \text{ k}\Omega} V_B = 20 \text{ mA}$$

$$\frac{1}{1 \text{ k}\Omega} V_A - \left[\frac{1}{2 \text{ k}\Omega} + \frac{1}{1.5 \text{ k}\Omega} \right] V_B = -50 \text{ mA}$$

FACTOR OUT
-1 BEFORE
WRITING MATRIX
EQ.

$$\begin{bmatrix} 1.667 & -0.667 \\ -0.667 & 1.1667 \end{bmatrix} \times 10^{-3} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 20 \\ 50 \end{bmatrix} \times 10^{-3}$$

SOLUTION

ECE231: Electrical Circuits and Systems I - Fall 2016 Lecture 6: Node Voltage Analysis

Example 2 – Use Node Voltage Analysis to solve for all node voltages in Figure 2


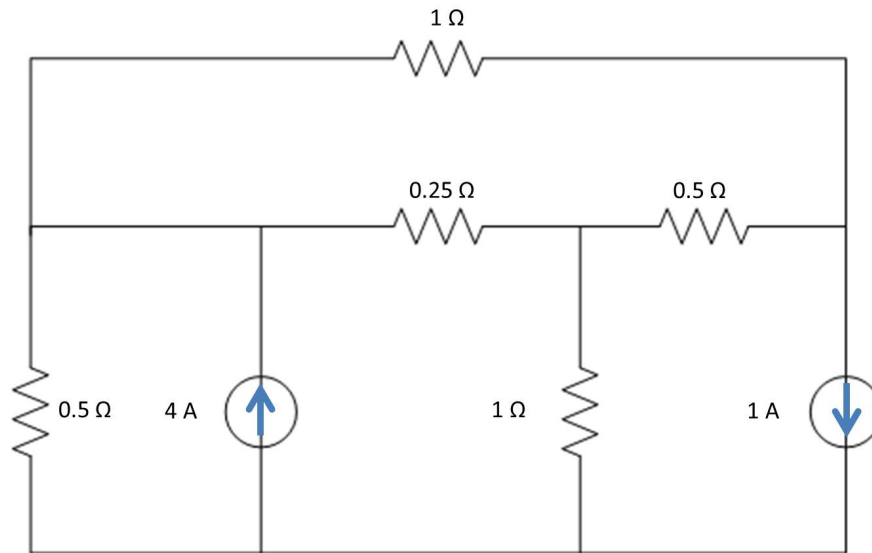


Figure 2: Circuit for Example 2

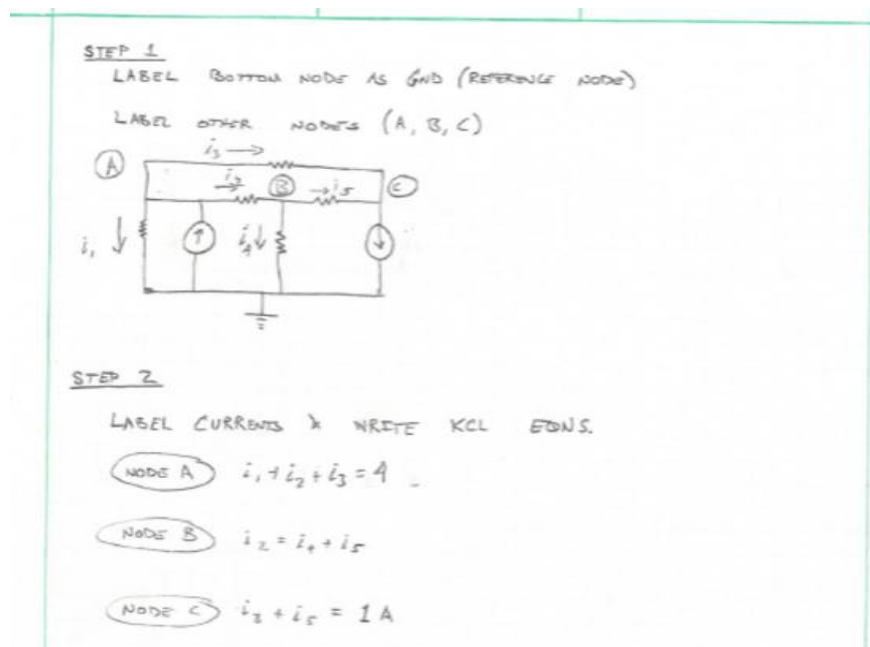

SOLUTION

ECE231: Electrical Circuits and Systems I - Fall 2016 Lecture 6: Node Voltage Analysis

STEP 3

WRITE UNKNOWN CURRENTS IN TERMS OF NODE VOLTAGES
& RESISTANCES

$$i_1 = \frac{V_A}{0.5}$$

$$i_2 = \frac{V_A - V_B}{0.25\Omega}$$

$$i_3 = \frac{V_A - V_C}{1\Omega}$$

$$i_4 = \frac{V_B}{1\Omega}$$

$$i_5 = \frac{V_B - V_C}{0.5\Omega}$$

STEP 3 (CONTINUED)

PLUG RESULTS INTO STEP 2 EQUATIONS

$$\textcircled{A} \frac{V_A}{0.5} + \frac{V_A - V_B}{0.25} + V_A - V_C = 4$$

$$\textcircled{B} \frac{V_A - V_B}{0.25} = V_B + \frac{V_B - V_C}{0.5}$$

$$\textcircled{C} V_A - V_C + \frac{V_B - V_C}{0.5} = 1A$$

STEP 4

REARRANGE INTO STANDARD FORM

$$\textcircled{A} 7V_A - 4V_B - 1 = 4$$

$$\textcircled{B} -4V_A + 7V_B - 2 = 0$$

$$\textcircled{C} -V_A - 2V_B + 3V_C = -1$$

$$\begin{bmatrix} 7 & -4 & -1 \\ -4 & 7 & -2 \\ -1 & -2 & 3 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} 4 \\ 0 \\ -1 \end{bmatrix}$$

$$V_A = 1.104 \text{ V}$$

$$V_B = 792 \text{ mV}$$

$$V_C = 563 \text{ mV}$$

SOLUTION

ECE231: Electrical Circuits and Systems I - Fall 2016

Lecture 6: Node Voltage Analysis


3 Node Voltage Analysis WITH Voltage Sources

When you have a voltage source in a circuit it will complicate Node Voltage Analysis slightly. This is because the first step in the process is to apply KCL at the nodes, but we cannot directly know the current into or out of an ideal voltage source. While it complicates the first step of the process, over all it will make most problems easier by reducing the number of node equations.


We will look at 3 different methods that can be used to solve these problems. You will need to understand all three, since they apply in different circumstances. Complex circuits may require you employ 2 or even all 3 of these methods.

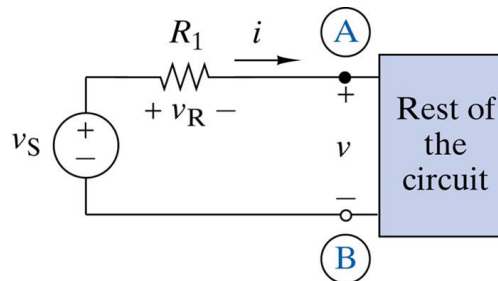3.1 Method 1: Source Transformation

If your voltage source is in series with a resistor, you should do a source transformation to get rid of your voltage source. You then revert back to the 4-step process for circuits without voltage sources. Figure 3 shows a reminder on how to transform voltage sources.



Circuit A

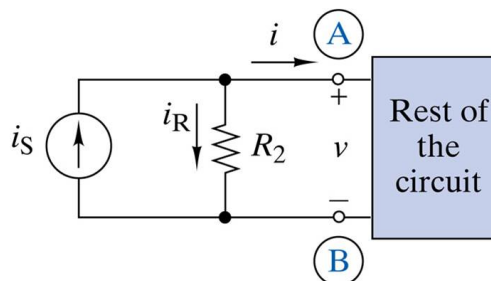

Circuit B

Figure 3: A quick reminder on source transformation

where i and v are related by

$$\begin{aligned} v_s &= i_s R_2 \\ i_s &= \frac{v_s}{R_1} \\ R_1 &= R_2 \end{aligned}$$

SOLUTION

ECE231: Electrical Circuits and Systems I - Fall 2016

Lecture 6: Node Voltage Analysis

Textbook Exercise 3-9: In Figure 4, use source transformation and Node Voltage Analysis to find the voltage across the $10\text{ k}\Omega$ resistor.

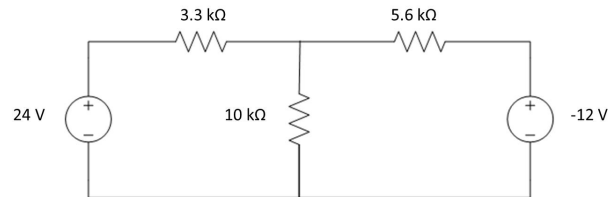


Figure 4: Circuit for Textbook Exercise 3-9

STEP 1
TRANSFORM VOLTAGE SOURCES

$I_{s1} = \frac{24}{3.3\text{k}} = 7.27\text{ mA}$ $I_{s2} = \frac{-12}{5.6\text{k}} = -2.14\text{ mA}$

STEP 2
WRITE KCL EQ FOR TOP NODE

$$(7.27 - 2.14)\text{ mA} = I_1 + I_2 + I_3$$
$$5.13\text{ mA} = \frac{V}{3.3\text{k}} + \frac{V}{10\text{k}} + \frac{V}{5.6\text{k}}$$
$$V = 5.13\text{ mA} \cdot \left[\frac{1}{3.3\text{k}} + \frac{1}{10\text{k}} + \frac{1}{5.6\text{k}} \right]^{-1}$$
$$V = 8.82\text{ V}$$

SOLUTION


ECE231: Electrical Circuits and Systems I - Fall 2016 Lecture 6: Node Voltage Analysis

3.2 Method 2: Smart choice of reference node

You should always think about what node makes the most sense as a reference node. When possible select one of the nodes that connects to your voltage source. By knowing that one side of the voltage source is grounded you will instantly know the voltage at the other source node.

Repeat Textbook Exercise 3-9 using Method 2

STEP 1
ASSIGN BOTTOM NODE AS GND.

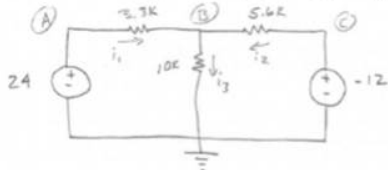

STEP 2
WRITE NODE VOLTAGE EQUATIONS FOR NODES A & C AND A KCL EQ FOR NODE B.

(A) $V_A = 24V$
(B) $i_1 + i_2 = i_3 = 0$
(C) $V_C = -12V$

STEP 3
WRITE CURRENT IN EQ (B) IN TERMS OF VOLTAGES & RESISTANCES.

$$i_1 = \frac{V_A - V_B}{3.3k} = \frac{24 - V_B}{3.3k}$$
$$i_2 = \frac{V_C - V_B}{5.6k} = \frac{-12 - V_B}{5.6k}$$
$$i_3 = \frac{V_B}{10k}$$

STEP 3 (CONT)
EQ (B) BECOMES

$$\frac{24}{3.3k} - \frac{V_B}{3.3k} - \frac{12}{5.6k} - \frac{V_B}{5.6k} - \frac{V_B}{10k} = 0$$

STEP 4
SOLVE FOR V_B

$$7.27 \times 10^{-3} - 2.19 \times 10^{-3} = V_B \left[\frac{1}{3.3k} + \frac{1}{5.6k} + \frac{1}{10k} \right]$$
$$V_B = 8.82V$$

SOLUTION

ECE231: Electrical Circuits and Systems I - Fall 2016 Lecture 6: Node Voltage Analysis

3.3 Method 3: Use a SuperNode

Method 3 is similar to method 2, except you do not have the reference node tied to your voltage sources. A *Supernode* is just a combination of the two nodes of a voltage source. The supernode equation is

$$v_s = v_a - v_b \quad (1)$$

where v_s is the source voltage and v_A & v_B are the node voltages on each side of the source.

Example: Use any combination of the three methods above to solve for I_0 in the circuit shown in Figure 5


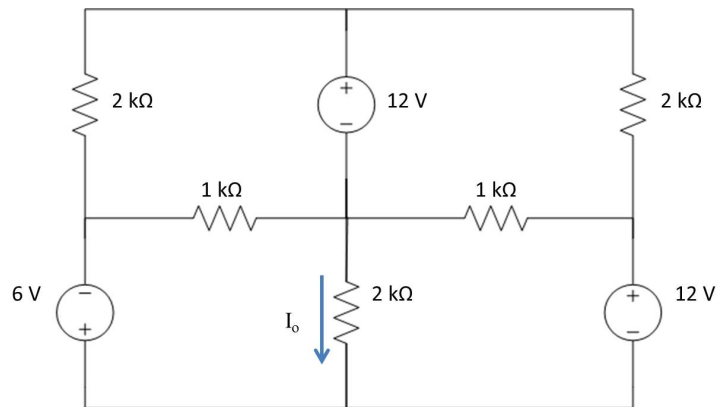


Figure 5: Circuit for Nodal Analysis Example

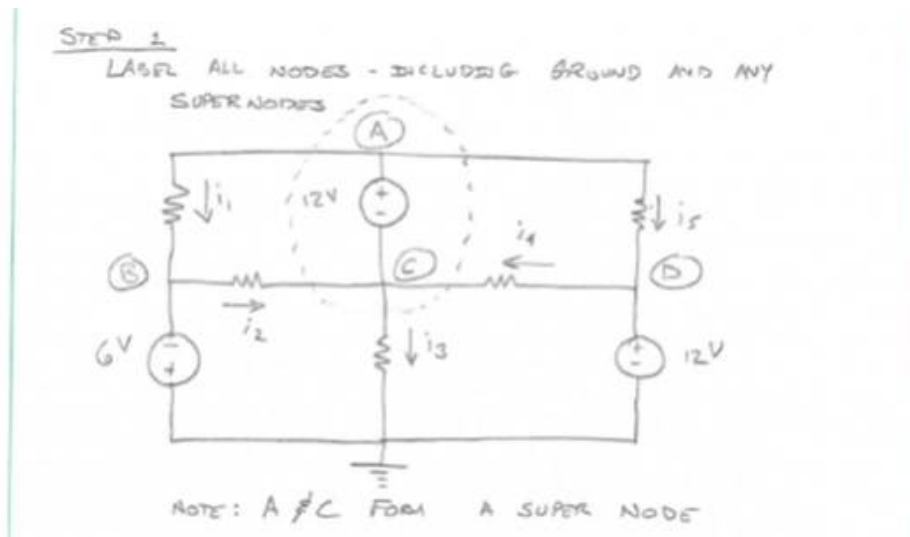

SOLUTION

ECE231: Electrical Circuits and Systems I - Fall 2016 Lecture 6: Node Voltage Analysis

STEP 2

WRITE NODE EQUATIONS

$$V_B = -6V$$

$$V_D = 12V$$

$$V_A - V_C = 12V \quad (\text{SUPER NODE})$$

$$i_1 - i_2 + i_3 - i_4 + i_5 = 0 \quad (\text{KCL @ SUPERNODE})$$

STEP 3

WRITE CURRENTS IN TERMS OF VOLTAGES & RESISTANCES

$$i_1 = \frac{V_A - V_B}{2k\Omega}$$

$$i_2 = \frac{V_B - V_C}{1k\Omega}$$

$$i_3 = \frac{V_C}{2k\Omega}$$

$$i_4 = \frac{V_D - V_C}{1k\Omega}$$

$$i_5 = \frac{V_A - V_D}{2k\Omega}$$

STEP 4

PLUG INTO KCL EQ.

$$\frac{V_A}{2k\Omega} - \frac{V_B}{2k\Omega} - \frac{V_B}{1k\Omega} + \frac{V_C}{1k\Omega} + \frac{V_C}{2k\Omega} - \frac{V_D}{1k\Omega} + \frac{V_C}{1k\Omega} + \frac{V_A}{2k\Omega} - \frac{V_D}{2k\Omega} = 0$$

PLUG IN FOR V_B & V_D . GROUP TERMS

$$-3mA + 6mA + 12mA - 6mA = V_A \left[\frac{2}{2k\Omega} \right] + V_C \left[\frac{1}{2k\Omega} + \frac{2}{1k\Omega} \right]$$

$$9mA = V_A \left[\frac{1}{1k\Omega} \right] + V_C \left[\frac{5}{2k\Omega} \right]$$

PLUG IN $V_A = 12 + V_C$

$$9mA = \frac{12}{1k\Omega} + \frac{V_C}{1k\Omega} + V_C \left[\frac{5}{2k\Omega} \right]$$

$$-3mA = V_C \left[\frac{7}{2k\Omega} \right]$$

$$V_C = -\frac{6}{7}V = -857mV$$

$$I_o = \frac{V_C}{2k\Omega} = -0.428mA$$

SOLUTION

ECE231: Electrical Circuits and Systems I - Fall 2016 Lecture 6: Node Voltage Analysis

4 Numerical Tools

You can quickly solve these by use Matlab. Going back to Exercise 3-4, we can do:

```
A = [1.667, -0.667; -0.667 1.667]*1e-3  
b = [20; 50]*1e-3  
x = inv(A)*b
```

You can also use the Python programming language:

```
import numpy as np  
A = np.array([[1.667, -0.667],[-0.667 1.667]])*1e-3  
b = np.array([20, 50])*1e-3  
x = inv(A).dot(b) # or x = np.linalg.solve(A,b)
```

Both are able to do numeric and symbolic manipulation.