

Lecture 21: RC and RL Circuit Natural Response

Upcoming events

1. Problem Set # 4 due Lesson 23
2. Homework # 5 due Lesson 25
3. Problem Set # 5 due Lesson 25
4. Quiz # 4 Lesson 26

OBJECTIVES:

1.

READING

Required :

- Textbook, section 7.1, pages 314–324

Optional : None

HOMEWORK

Required textbook problems : 7.7, 7.10 (for each problem derive each differential equation for $t > 0$ and solve using separation of variables)— Due Lesson 23

Recommended textbook problems : 7.11

1 A Brief Review of Differential Equations Solution Techniques

1.1 Separation of Variables

Let's look at the following first order, homogenous differential equation:

$$\frac{\partial v(t)}{\partial t} + \frac{1}{RC}v(t) = 0 \quad (1)$$

We can rewrite this as:

$$\frac{1}{v(t)}\partial v(t) = -\frac{1}{RC}\partial t \quad (2)$$

where we have separated the variables, meaning that we have gathered every term that has a $v(t)$ on one side and the other stuff on the other side.

Now we integrate both sides:

$$\int \frac{1}{v(t)}\partial v(t) = -\int \frac{1}{RC}\partial t \quad (3)$$

$$\ln v(t) + K_1 = -\frac{t}{RC} + K_2 \quad (4)$$

but we can combine our constants

$$\ln v(t) = -\frac{t}{RC} + K \quad (5)$$

where $K = K_2 - K_1$, but really it is just a constant....

SOLUTION

ECE231: Electrical Circuits and Systems I - Spring 2016 Lecture 21: RC and RL Circuit Natural Response

Solving for $v(t)$ gives

$$v(t) = e^{-\frac{t}{RC} + K} \quad (6)$$

but this simplifies to

$$v(t) = K' e^{-\frac{t}{RC}} \quad (7)$$

where $K' = e^K$

The value of K' can be found using initial conditions.

1.2 Undetermined Coefficients

Let's start with the same differential equation from above:

$$\frac{\partial v(t)}{\partial t} + \frac{1}{RC}v(t) = 0 \quad (8)$$

Any solution to this equation has to be linearly proportional to the derivative of itself. We can state this mathematically by rearranging the equation:

$$\frac{\partial v(t)}{\partial t} = -\frac{1}{RC}v(t) \quad (9)$$

What function do we know that the derivative has the same form as the original function?

The exponential function

So, let's guess a solution of the form:

$$v(t) = K e^{st} \quad (10)$$

Now, we can plug that into our original differential equation:

$$\frac{\partial K e^{st}}{\partial t} = -\frac{1}{RC} K e^{st} \quad (11)$$

Take the derivative:

$$K s e^{st} = -\frac{1}{RC} K e^{st} \quad (12)$$

Therefore

$$s = -\frac{1}{RC} \quad (13)$$

$$v(t) = K e^{-\frac{t}{RC}} \quad (14)$$

Same as before!

K is found using initial conditions. More on that later....

SOLUTION

2 RC & RL Circuit Analysis

Let's start by writing the differential equations for a couple of simple circuits:

Example 1 – Write the differential equations for the circuits shown in Figure 1

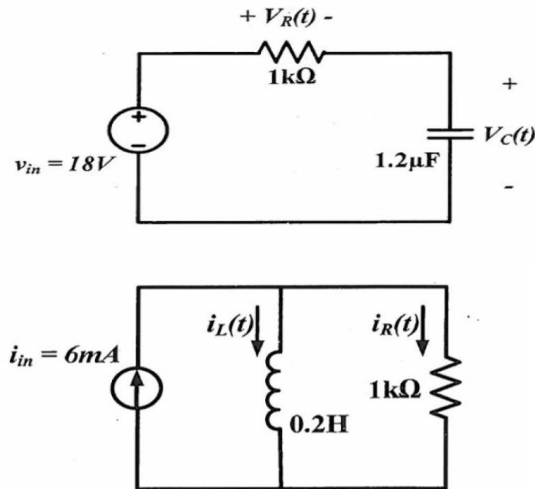


Figure 1: Circuits for Example 1

Circuit #1

$$v_r(t) + v_c(t) = 18 \text{ V}$$

$$i_r(t)R + v_c(t) = 18 \text{ V}$$

but $i_r(t) = i_c(t)$, therefore

$$i_c(t)R + v_c(t) = 18 \text{ V}$$

$$CR \frac{\partial v_c(t)}{\partial t} + v_c(t) = 18 \text{ V}$$

$$\frac{\partial v_c(t)}{\partial t} + \frac{1}{RC} v_c(t) = \frac{1}{RC} 18 \text{ V}$$

Circuit #2

$$i_L(t) + i_R(t) = 6 \text{ mA} \quad (15)$$

$$i_L(t) + \frac{v_R(t)}{R} = 6 \text{ mA} \quad (16)$$

but since $v_R(t) = v_L(t)$

$$i_L(t) + \frac{v_L(t)}{R} = 6 \text{ mA} \quad (17)$$

$$i_L(t) + \frac{L}{R} \frac{\partial i_L(t)}{\partial t} = 6 \text{ mA} \quad (18)$$

$$\frac{\partial i_L(t)}{\partial t} + \frac{R}{L} i_L(t) = \frac{R}{L} 6 \text{ mA} \quad (19)$$

SOLUTION

ECE231: Electrical Circuits and Systems I - Spring 2016 Lecture 21: RC and RL Circuit Natural Response

When analyzing RC or RL circuits, the analysis can be broken into three parts:

1. *Steady state ($t < 0$), leading up to our initial conditions. Usually we consider the circuit to have been in this state for a “long time”*
2. *Transient Response. This is the interesting part..... and the part we are most interested in. This is where the dynamic element (Capacitor or Inductor) has an impact on the circuit*
3. *Steady state..... After some time our circuit element will return to steady state*

Additionally, we can look at two types of circuit responses:

Natural Response – *This is the response to a homogenous differential equation. For $t > 0$, there are no sources in the circuit; only the initial conditions drive the response.*

Forced Response – *This is the response to a non-homogenous differential equations; this means for $t > 0$ there are sources in the circuit. Typically initial conditions are set to zero when looking at forced response.*

Today we will look at natural response and will deal with forced responses next lesson.

Let's first look at a simple circuit that shows the time response of a discharging capacitor. See Figure 2.

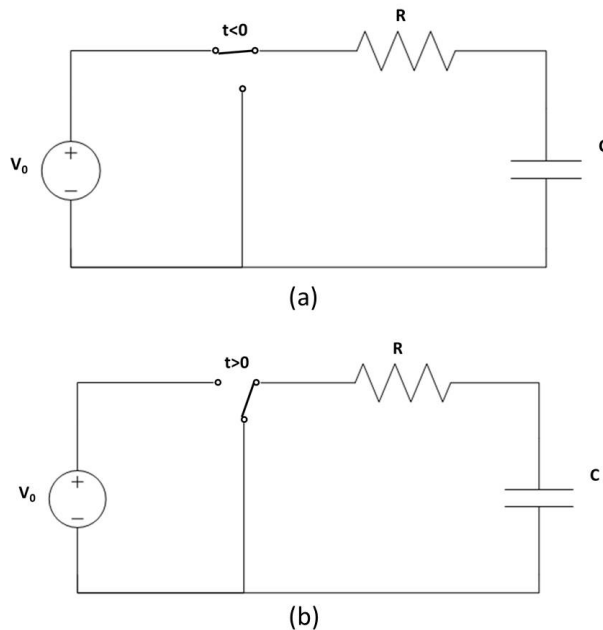


Figure 2: (a) The circuit before the switch is moved (b) the final circuit, after switch is moved

Before we move the switch, the voltage across the capacitor equals V_0 ; we are assuming the switch has been in this position for a long time (we will talk more about what a long time really means).

At $t = 0$ we move the switch and enter the *Transient Response* phase of our analysis. The differential equation for this circuit will look like (this is easily found using KVL):

$$\frac{\partial v_c(t)}{\partial t} + \frac{1}{RC}v_c(t) = 0 \quad (20)$$

From before we found that the solution to these differential equations have the form:

$$v_c(t) = K e^{-\frac{t}{RC}} \quad (21)$$

SOLUTION

ECE231: Electrical Circuits and Systems I - Spring 2016 Lecture 21: RC and RL Circuit Natural Response

To find K we use our initial condition:

$$v_c(0) = V_0$$

which give us:

$$K = V_0$$

So our final circuit response is:

$$v_c(t) = V_0 e^{-\frac{t}{RC}}$$

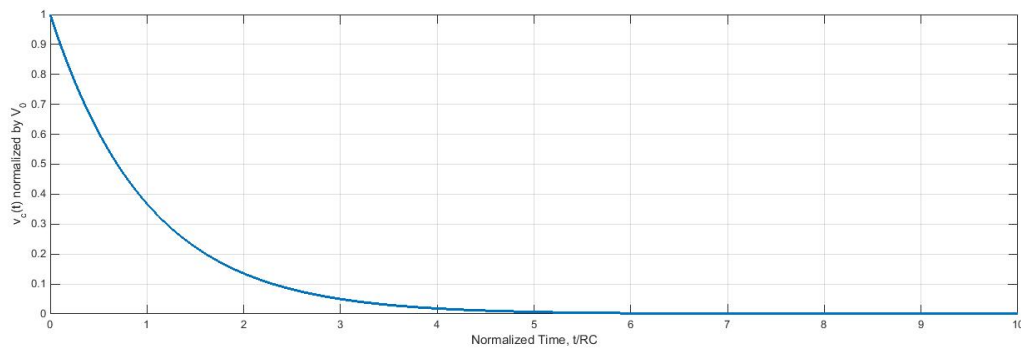


Figure 3: Capacitor Natural Response

What can we learn from this?

First, we should recognize that this is a decaying exponential function, that starts at V_0 and decays to zero. Second we can see that it is effective zero at time $t = \frac{5}{RC}$. Recalling from our initial discussion on exponential functions, they go to zero after approximately five time constants. This leads us to define a time constant, T_C for the RC circuit:

$$T_C = RC$$

So to tie this back to our three analysis phases, we see that for $t < 0$, the circuit is in a steady state with a fully charged capacitor. For $0 < t < \frac{5}{RC}$ the circuit is in the transient response phase with the capacitor discharging. For $t > \frac{5}{RC}$ the circuit has returned to a steady state condition.

SOLUTION

ECE231: Electrical Circuits and Systems I - Spring 2016 Lecture 21: RC and RL Circuit Natural Response

We can now examine the analogous case for an inductor. See Figure 4.

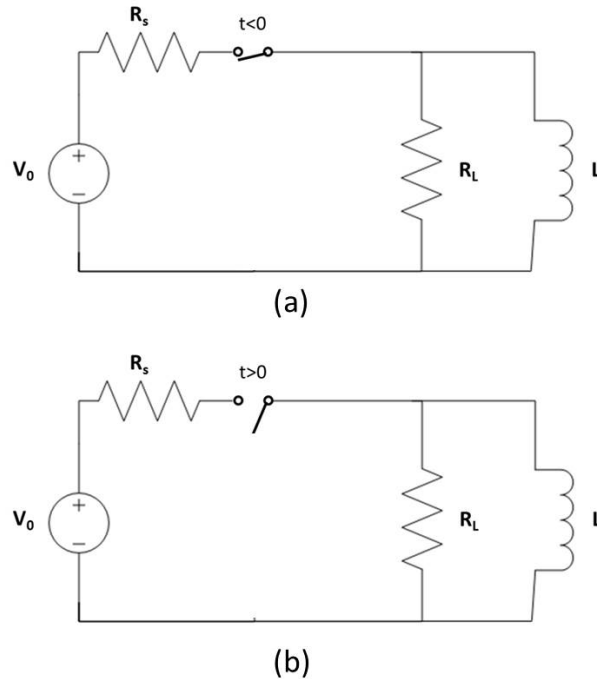


Figure 4: (a) The circuit before the switch is moved (b) the final circuit, after switch is moved

What is the current through the inductor for $t < 0$?

There are a couple of steps or methods to figure this out, but first you have to recall that for steady state D.C. an inductor looks like a short. This means R_L has no impact on the circuit for $t < 0$ since it is shorted out.

Next you simply use Ohm's Law to find the current around the loop (which now effectively contains the voltage source and R_s). This is effectively a source transformation:

$$i_L(t \leq 0) = \frac{V_0}{R_s}$$

Later this will serve as our initial condition.

The differential equation for $t > 0$ is:

$$\frac{\partial i_L(t)}{\partial t} + \frac{R_L}{L} i_L(t) = 0$$

Which one again we know the solution has to have the form:

$$i_L(t) = K e^{st}$$

s is just a dummy variable which we can solve for:

$$\begin{aligned} \frac{\partial i_L(t)}{\partial t} &= -\frac{R_L}{L} i_L(t) \\ \frac{\partial K e^{st}}{\partial t} &= K s e^{st} = -\frac{R_L}{L} K e^{st} \end{aligned}$$

Therefore

$$s = -\frac{R_L}{L}$$

SOLUTION

ECE231: Electrical Circuits and Systems I - Spring 2016 Lecture 21: RC and RL Circuit Natural Response

Finally K is found using our initial condition:

$$K = \frac{V_0}{R_s}$$

So our circuit natural response is

$$i_L(t) = \frac{V_0}{R_s} e^{-\frac{R_L}{L}t}$$

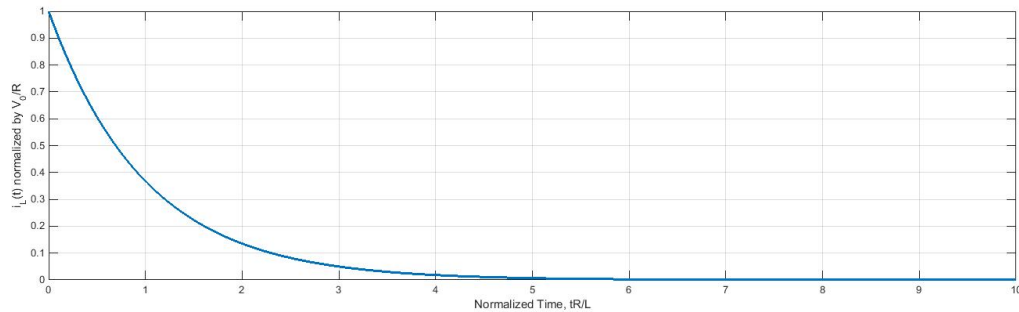


Figure 5: Inductor Natural Response

What you should be able to interpret from this equation and graph is:

$$T_L = \frac{L}{R_L}$$

Where T_L is the time constant for an RL circuit.

Notice this response is the same as the capacitor response (a decaying exponential); the only difference is the capacitor vertical axis is voltage and this inductor vertical axis is current.

SOLUTION

ECE231: Electrical Circuits and Systems I - Spring 2016 Lecture 21: RC and RL Circuit Natural Response

Example 2 – For the circuit shown in Figure 6, find $v_c(t)$ and $i(t)$

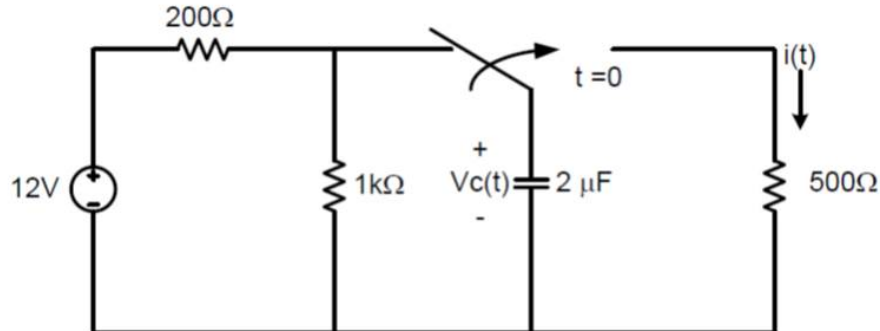


Figure 6: Example 2 Circuit

Assume the switch has been in position 1 long enough for the circuit to reach steady state and find the voltage across the capacitor. This will be our initial condition, $v_c(0)$. Since at steady state, a capacitor acts like an open circuit to DC, we can find $v_c(0)$ by a simple voltage divider:

$$v_c(0) = \frac{1 \text{ k}\Omega}{1 \text{ k}\Omega + 200 \Omega} 12 \text{ V} = 10 \text{ V}$$

For $t > 0$, the circuit is only the rightmost resistor in a loop with the capacitor. We can write a KVL equation for that loop:

$$v_c(t) - v_R(t) = 0$$

which equals

$$v_c(t) - i_R(t)R = 0$$

but we also know that $i_R(t) = -i_c(t)$ (watch signs using passive sign convention) and that

$$i_c(t) = C \frac{\partial v_c(t)}{\partial t}$$

which gives

$$v_c(t) + RC \frac{\partial v_c(t)}{\partial t} = 0$$

rearranging gives

$$\frac{\partial v_c(t)}{\partial t} + \frac{1}{RC} v_c(t) = 0$$

We know the solution of this differential equation is:

$$v_c(t) = v_c(0) \times e^{-\frac{1}{RC}t}$$

plugging in for $v_c(0) = 10 \text{ V}$, $R = 500 \Omega$ and $C = 2 \mu\text{F}$ gives:

$$v_c(t) = 10e^{-1000t}u(t)$$

Where the $u(t)$ accounts for the fact that this solution is only valid for $t > 0$

We can find $i(t)$ by using Ohm's law

$$i(t) = \frac{v_c(t)}{R} = 20e^{-1000t}u(t) \text{ mA}$$

you could also have found $i(t)$ by

$$i_c(t) = C \frac{\partial v_c(t)}{\partial t}$$

SOLUTION

ECE231: Electrical Circuits and Systems I - Spring 2016 Lecture 21: RC and RL Circuit Natural Response

Example 3 – For the circuit shown in Figure 7, find $v_c(t)$ and $i(t)$

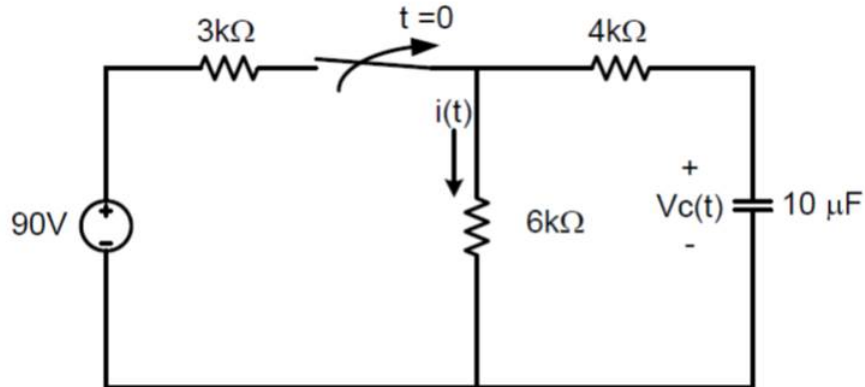


Figure 7: Example 3 Circuit

Like the previous example we can find the initial capacitor voltage, $v_c(0^-)$, by using a voltage divider:

$$v_c(0) = \frac{6 \text{ k}\Omega}{3 \text{ k}\Omega + 6 \text{ k}\Omega} 90 \text{ V} = 60 \text{ V}$$

Notice the $4 \text{ k}\Omega$ resistor had no impact on the initial capacitor voltage since at steady state there is no current through it, therefore, no voltage is dropped across it.

Similar to the last example, when the switch is moved, the new circuit contains no sources, just a capacitance and resistance. For $t > 0$, $R_{eq} = 10 \text{ k}\Omega$ and $C = 10 \text{ }\mu\text{F}$.

The differential equation for the circuit is:

$$\frac{\partial v_c(t)}{\partial t} + \frac{1}{RC} v_c(t) = 0$$

and the solution has the form:

$$v_c(t) = v_c(0) \times e^{-\frac{1}{RC}t}$$

plugging in for $v_c(0) = 60 \text{ V}$, $R = 10 \text{ k}\Omega$ and $C = 10 \text{ }\mu\text{F}$ gives:

$$v_c(t) = 60e^{-10t}u(t) \text{ V}$$

We can find $i(t)$ by using Ohm's law

$$i(t) = \frac{v_c(t)}{R} = 6e^{-10t}u(t) \text{ mA}$$

SOLUTION

ECE231: Electrical Circuits and Systems I - Spring 2016 Lecture 21: RC and RL Circuit Natural Response

Example 4 – For the circuit shown in Figure 8, find $v_c(t)$ and $i(t)$

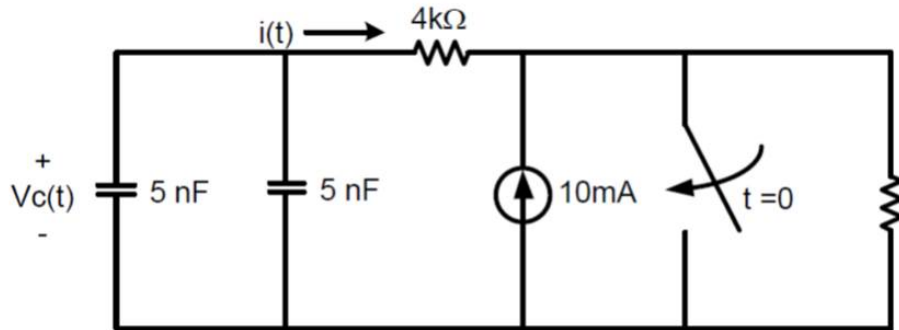


Figure 8: Example 4 Circuit

STEP 1 - DO A SOURCE TRANSFORMATION & COMBINE CAPACITORS

NOW IT IS JUST LIKE THE TWO EXAMPLES BEFORE

$v_c(0^-) = 50V$ - FOR $t < 0$ NO CURRENT FLOWS IN EITHER RESISTOR!

$$\frac{dv_c(t)}{dt} + \frac{1}{RC} v_c(t) = 0$$

SOLUTION

$$v_c(t) = v_c(0^-) e^{-\frac{t}{RC}}$$

$$v_c(t) = 50 e^{-25,000 t} u(t) V$$

$$i(t) = \frac{50}{4k} e^{-25k t} u(t) A$$

$$i(t) = 12.5 e^{-25,000 t} u(t) mA$$

$R = 4k\Omega$
 $C = 10nF$

SOLUTION

ECE231: Electrical Circuits and Systems I - Spring 2016 Lecture 21: RC and RL Circuit Natural Response

Example 5 –For our last example, let's tackle an inductor circuit.....

For the circuit shown in Figure 9, find $i_L(t)$ and $v(t)$

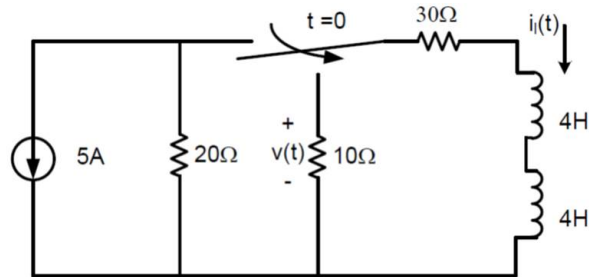


Figure 9: Example 5 Circuit

FOR $t < 0$,

- RECALL: INDUCTORS LOOK LIKE SHORTS TO DC!

$$i_L(0^-) = -\frac{20}{50} 5 = -2A$$

FOR $t > 0$

$R_T = 40\Omega$

- INDUCTORS IN SERIES ADD

$$V_L(t) = L \frac{di_L(t)}{dt}$$

$$-i_R(t) + i_L(t) = 0$$

$$-\frac{V_L(t)}{R_T} + i_L(t) = 0$$

$$-\frac{L}{R_T} \frac{di_L(t)}{dt} + i_L(t) = 0$$

$$\frac{di_L(t)}{dt} - \frac{R_T}{L} i_L(t) = 0$$

SOLUTION

$$i_L(t) = i_L(0^-) e^{-\frac{R_T}{L} t}$$

$$i_L(t) = -2 e^{-5t} u(t) A$$

$$v(t) = -20 e^{-5t} u(t) V$$